


RWE Denizli-Kaklık Gas Power Plant: 775 MW



by
Prof. Dr. Osman SEVAİOĞLU
Electrical and Electronics Engineering Department

Voltage Waveform


Consider the following AC circuit driven by a source with an AC voltage waveform;

$$V(t) = V_{max} \cos \omega t$$

Voltage phasor will then be


$$V_{max} \angle 0^\circ$$

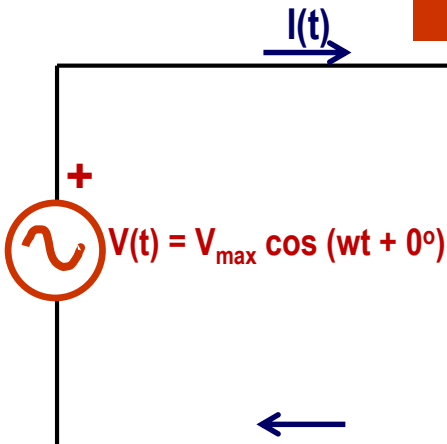For simplicity, phase angle of the voltage waveform is assumed to be zero



$$\text{Load} = R + jX \\ = Z \angle \theta$$
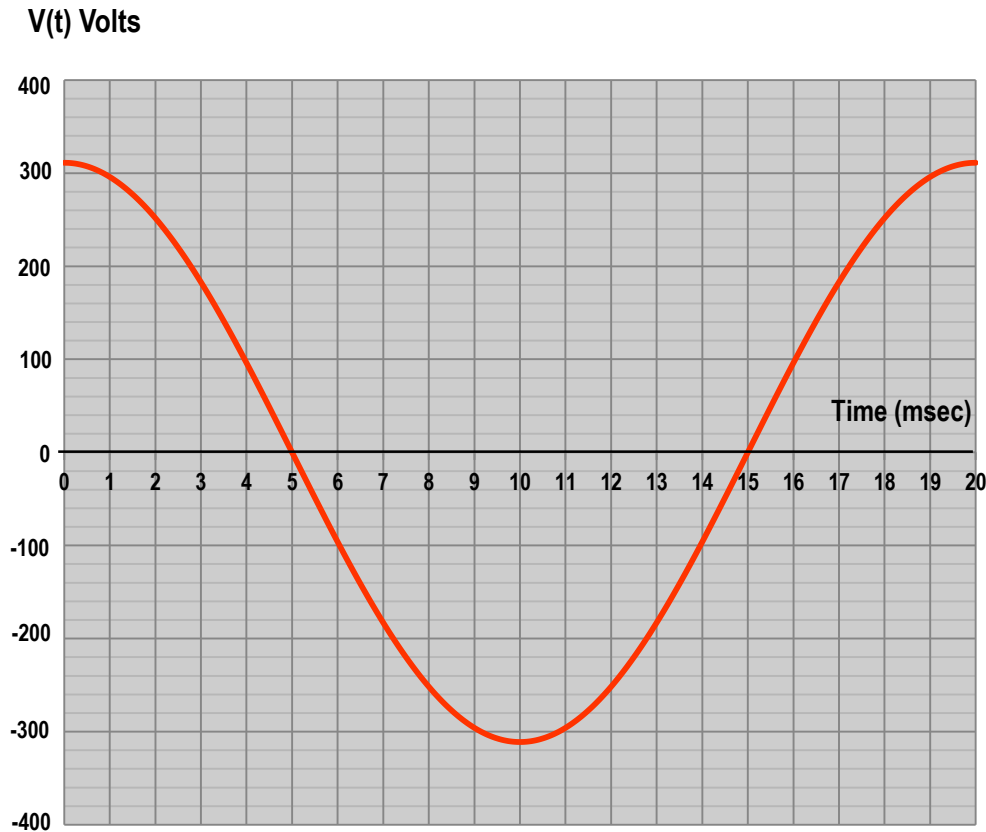
$$Z = \sqrt{R^2 + X^2}, \quad \theta = \tan^{-1}(X/R)$$






Current Waveform

Current Phasor

$$I = \frac{V_{max} \angle 0^\circ}{Z \angle \theta} = I_{max} \angle -\theta$$

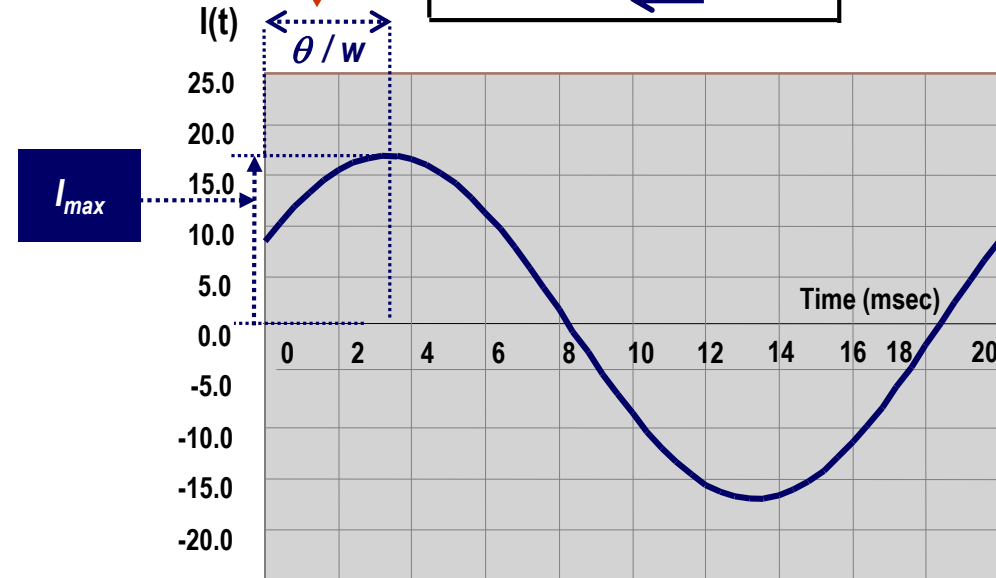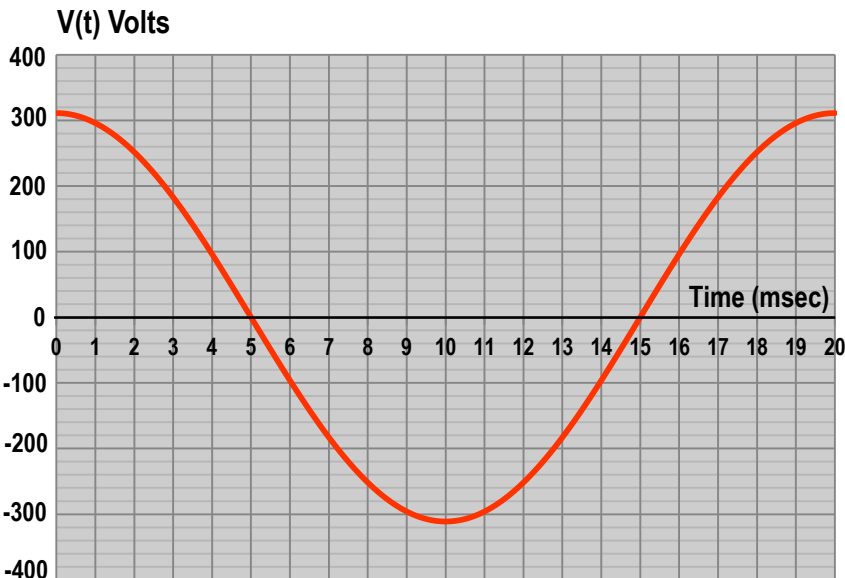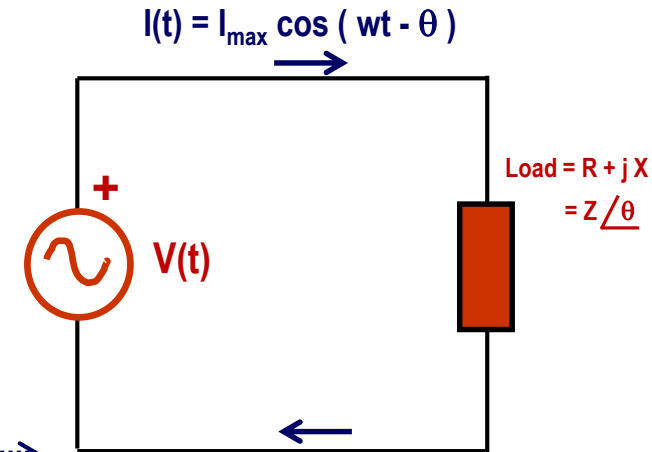Phase (time) shift;
 $t_1 = \theta_1 / \omega = 3.5 \text{ msec}$




Current Waveform

Current phasor will then be

$$I_{max} \angle -\theta$$


Current waveform will then be

$$I(t) = I_{max} \cos (wt - \theta)$$

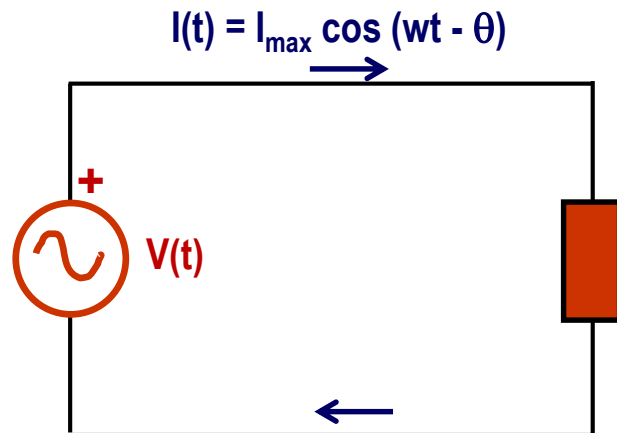

$$\begin{aligned} \text{Load} &= R + jX \\ &= Z \angle \theta \end{aligned}$$


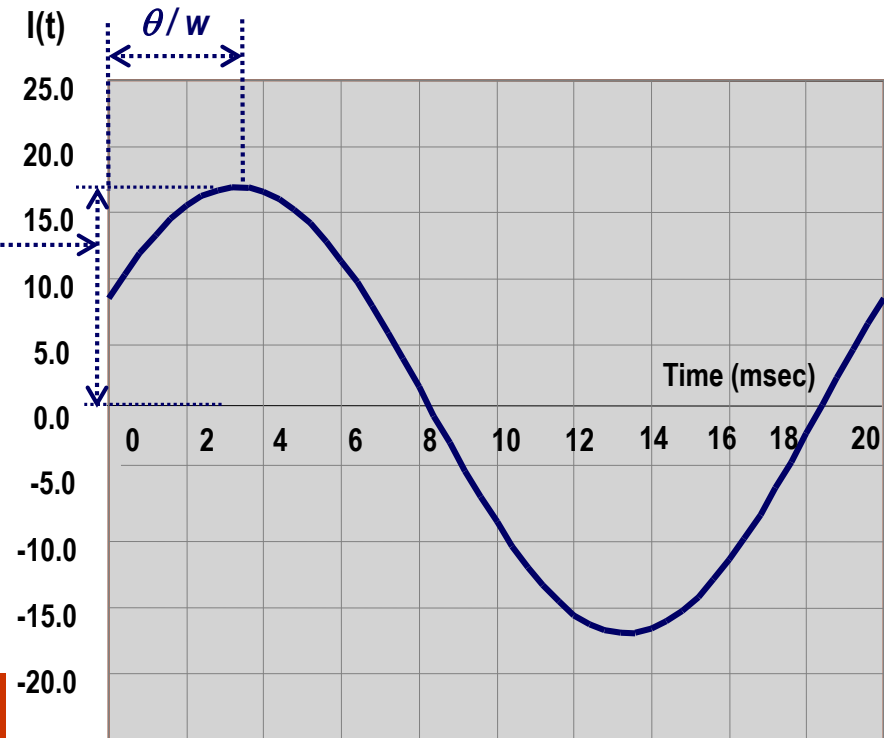
$$Z = \sqrt{R^2 + X^2}, \quad \theta_l = \tan^{-1} (X / R)$$



Voltage and Current Waveforms

Please note that the angle difference; θ depends only on the resistance R and reactance X of the load

$$\theta = \tan^{-1} (X / R)$$

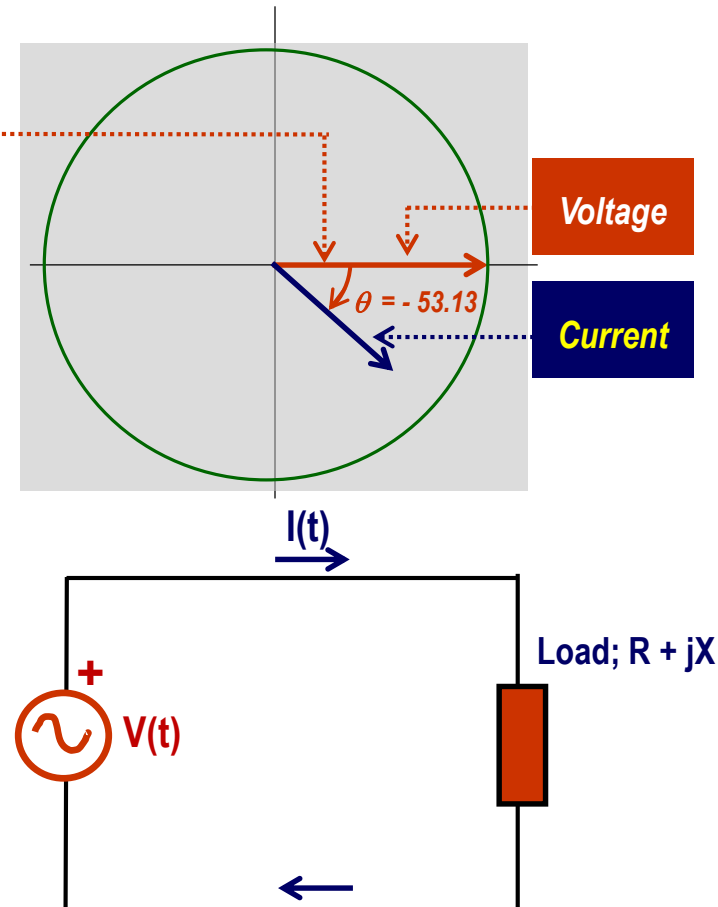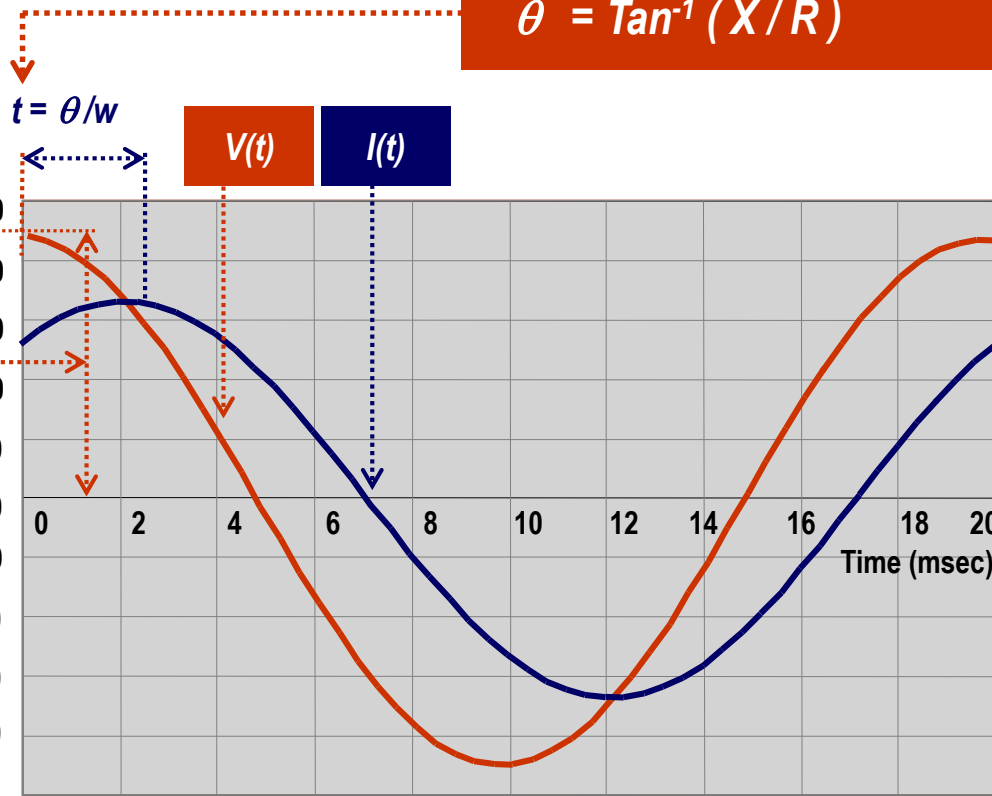

AC Power - Power Expression

Voltage and current waveforms are

$$V(t) = V_{max} \cos wt$$

$$I(t) = I_{max} \cos (wt - \theta)$$


Power waveform will then be

$$S(t) = V(t) \times I(t)$$

$$= V_{max} \cos wt \times I_{max} \cos (wt + \theta)$$

Please note that;
“-” sign here should be altered to “+” due to the conjugation operator in the definition of power:

$$S = V \times I^*$$

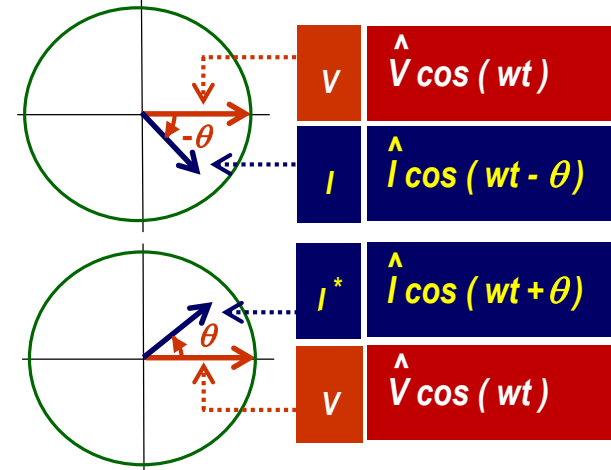

$$\cos(a + b) = \cos a \cos b - \sin a \sin b$$


V_{max}

$$\cos(a - b) = \cos a \cos b + \sin a \sin b$$

$V(t)$

$$\cos(a + b) + \cos(a - b) = 2 \cos a \cos b$$
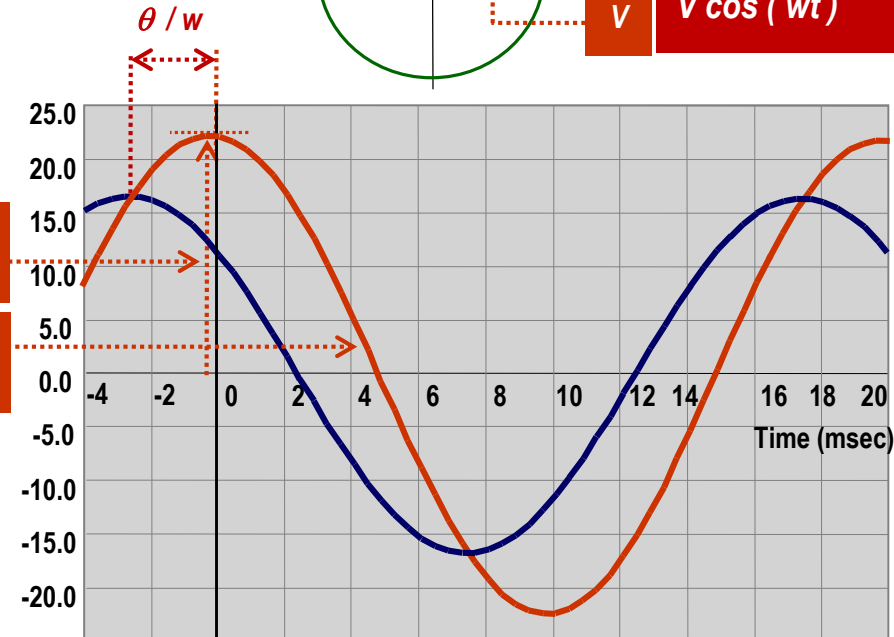
$$\cos a \cos b = \frac{1}{2} [\cos(a + b) + \cos(a - b)]$$



AC Power - Power Expression


Power waveform is the product of the voltage and conjugate (the phase angle with + sign) of the current waveforms

$$S(t) = V_{\max} I_{\max} \cos wt \times \cos (wt + \theta)$$

$$\cos a \times \cos b = \frac{1}{2} [\cos (a + b) + \cos (a - b)]$$

$$\begin{aligned} S(t) &= \frac{1}{2} V_{\max} I_{\max} [\cos (wt + wt + \theta) + \cos (wt - wt - \theta)] \\ &= \frac{1}{2} V_{\max} I_{\max} [\cos (2wt + \theta) + \cos \theta] \\ &= (V_{\max} / \sqrt{2}) (I_{\max} / \sqrt{2}) [\cos (2wt + \theta) + \cos \theta] \\ &= V_{\text{rms}} I_{\text{rms}} [\cos (2wt + \theta) + \cos \theta] \end{aligned}$$
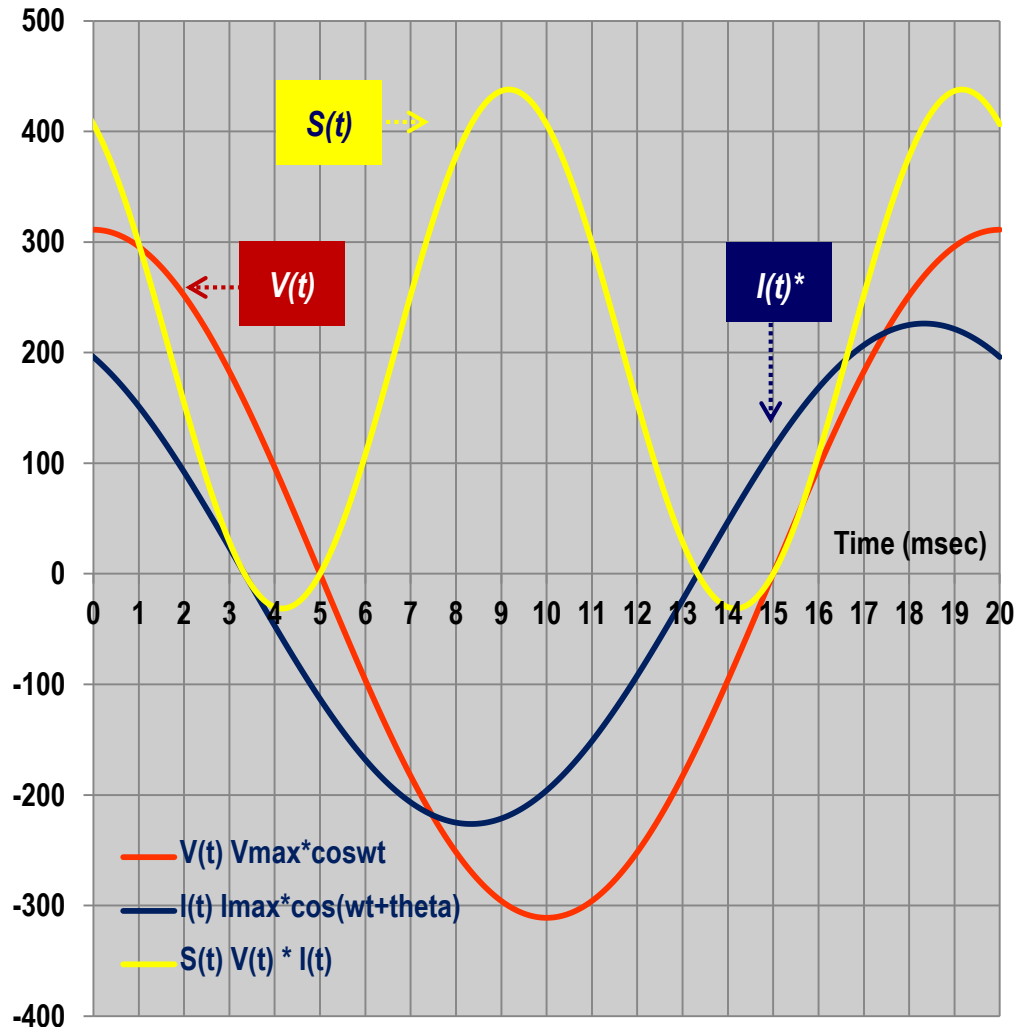
$$V_{\text{rms}} = V_{\max} / \sqrt{2} \quad \theta = \theta_v - \theta_i = \tan^{-1}(X/R)$$






AC Power – Decomposition of Power Expression

Power given in the above expression may be decomposed into two components;

$$S(t) = V_{rms} I_{rms} \cos(2\omega t + \theta) + V_{rms} I_{rms} \cos \theta$$

Sinusoidal (AC) Term

Constant (DC) Term

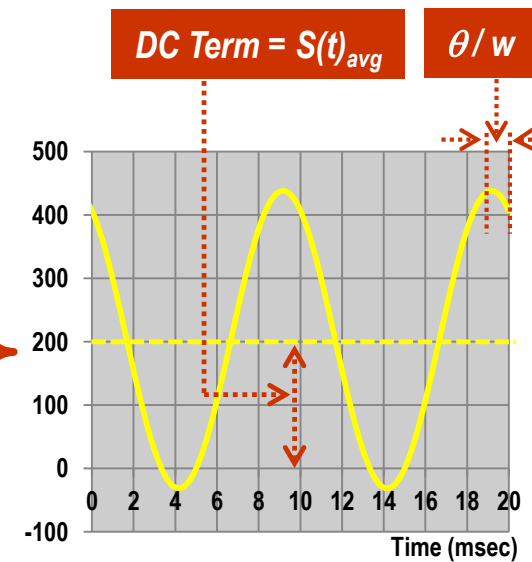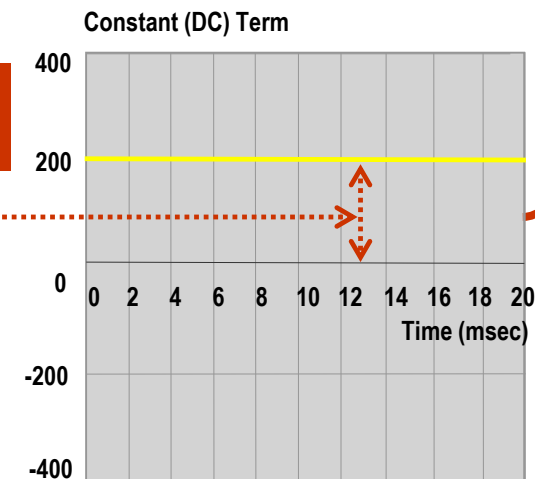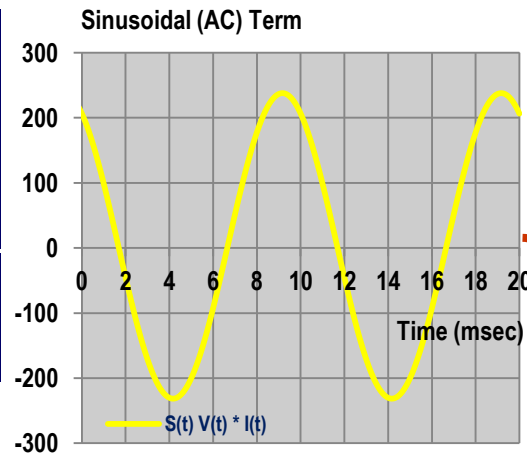

AC Power – Average Power Expression

Average Power

$$S(t) = V_{rms} I_{rms} [\cos(2\omega t + \theta) + \cos \theta]$$

$$S(t)_{avg} = (1/T) \int_0^T S(t) dt$$



$$\begin{aligned} S(t)_{avg} &= (1/T) \int P(t) dt \\ &= (1/T) \int V_{rms} I_{rms} [\cos(2\omega t + \theta) + \cos \theta] dt \\ &= (1/T) \int V_{rms} I_{rms} \cos(2\omega t + \theta) dt + (1/T) \int V_{rms} I_{rms} \cos \theta dt \end{aligned}$$

= 0

Constant (DC) Term

Average is zero

Sum of these areas is zero

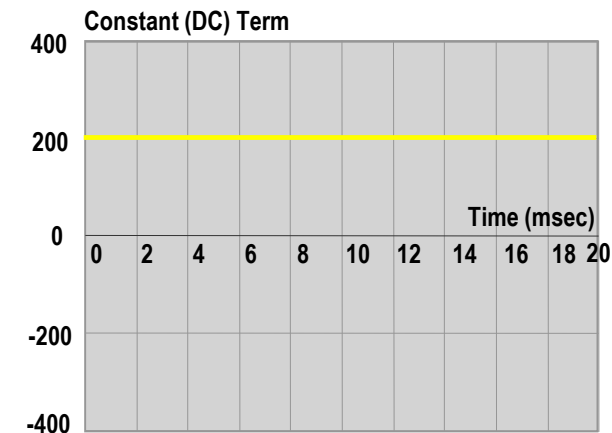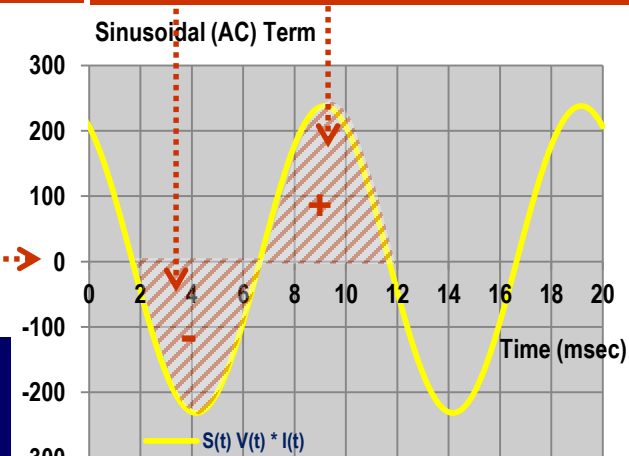


AC Power – Average Power Expression

Average Power


$$\begin{aligned}
 S(t)_{avg} &= (1/T) \int P(t) dt \\
 &= (1/T) V_{rms} I_{rms} \int \cos \theta dt \\
 &= (1/T) V_{rms} I_{rms} \cos \theta \int dt \quad \leftarrow \int_0^T dt = T \\
 &= (1/T) T V_{rms} I_{rms} \cos \theta \\
 &= V_{rms} I_{rms} \cos \theta
 \end{aligned}$$

$$S(t)_{avg} = V_{rms} I_{rms} \cos \theta$$

Please note that θ is constant

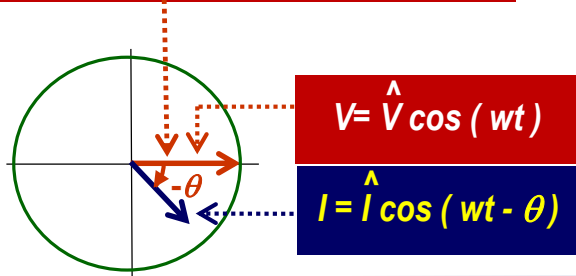


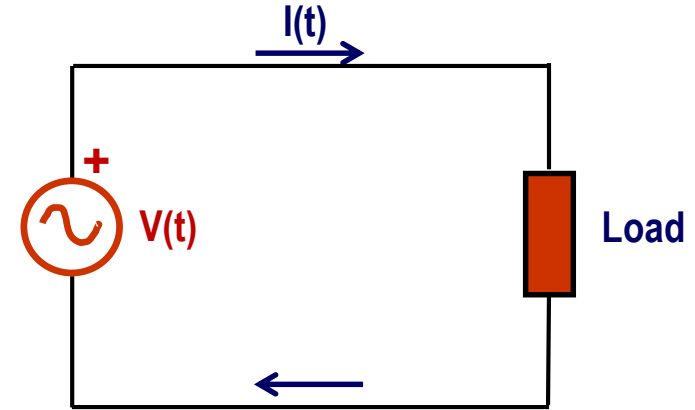Most of the students forget to put this multiplier term in their formula, during the examinations. Please be careful!



DC Term = $S(t)_{avg}$

θ/w

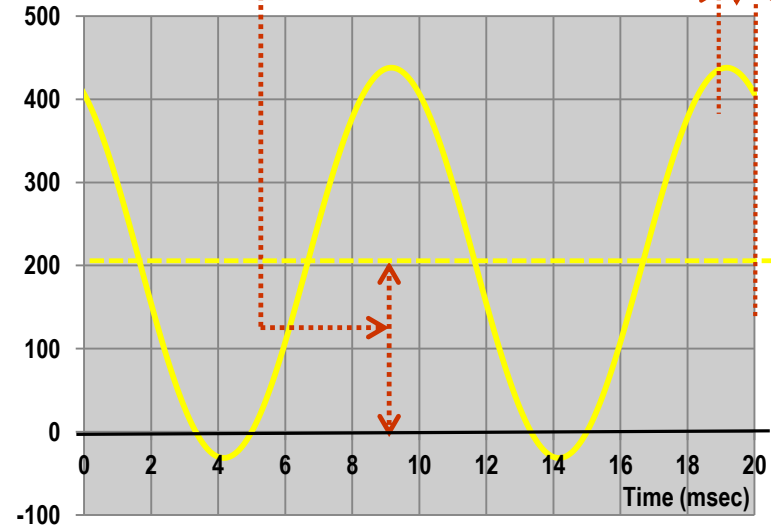

Example



Question

Calculate the average and instantaneous powers dissipated in the load shown in the following circuit;

System Parameters:

$$V_{rms} = 100 \text{ Volts}$$
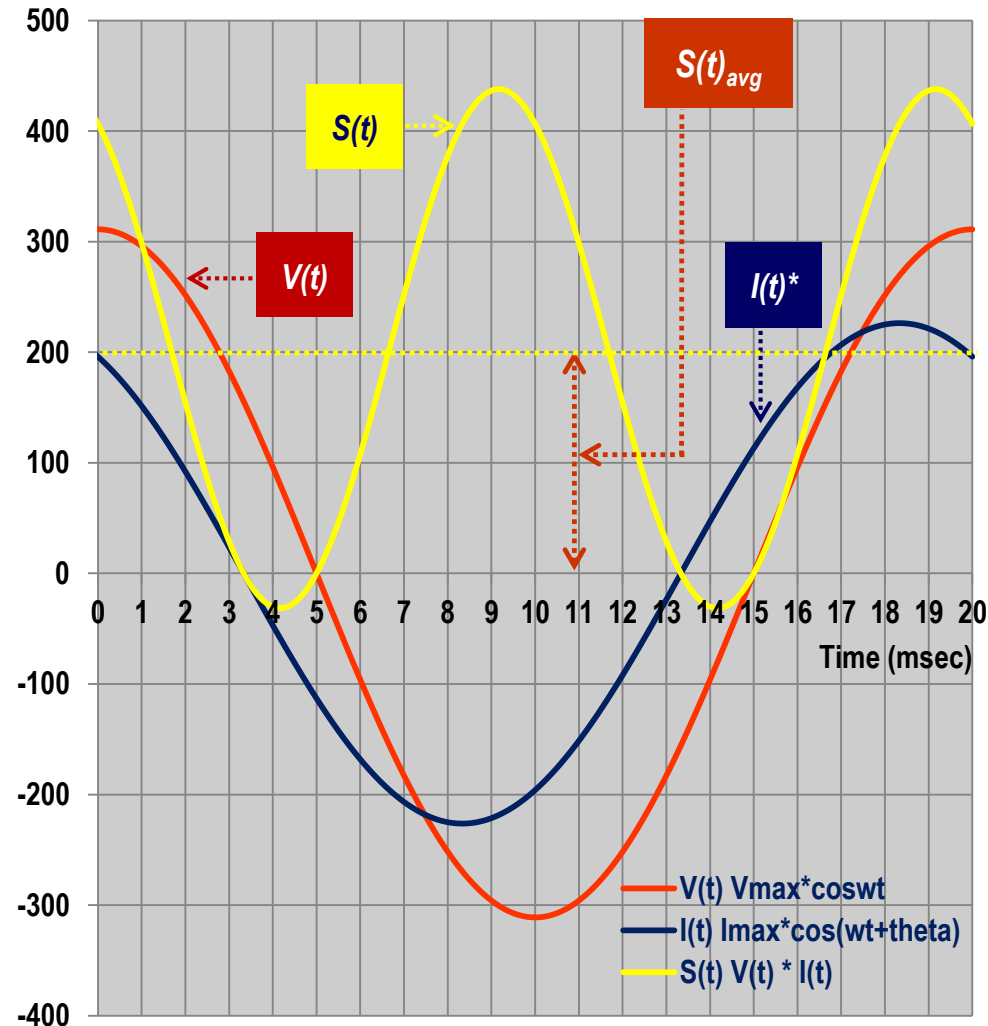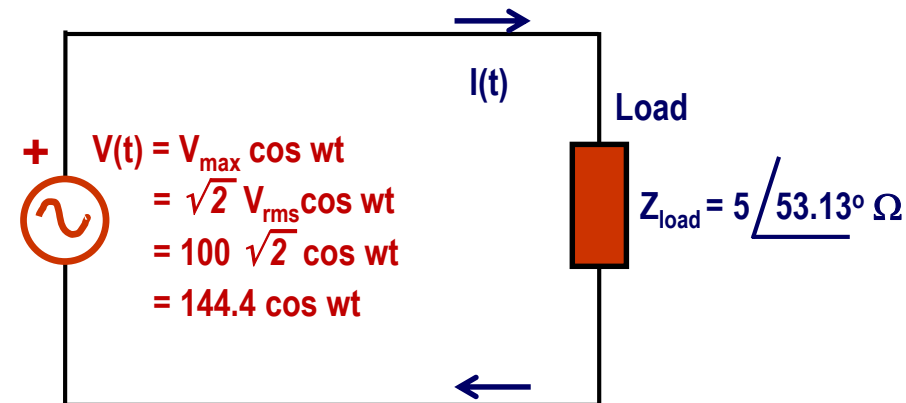
$$Z_{load} = 3 + j4 \text{ Ohms} = 5 \angle 53.13^\circ \text{ Ohms}$$




Solution


$$V_{max} = 100 \times \sqrt{2} = 144.4 \text{ Volts}$$

$$\begin{aligned} I &= V_{max} \angle 0^\circ / Z \angle \theta \\ &= 144.4 \angle 0^\circ / 5 \angle 53.13^\circ \\ &= 28.8 \angle -53.13^\circ \text{ Amp} \end{aligned}$$
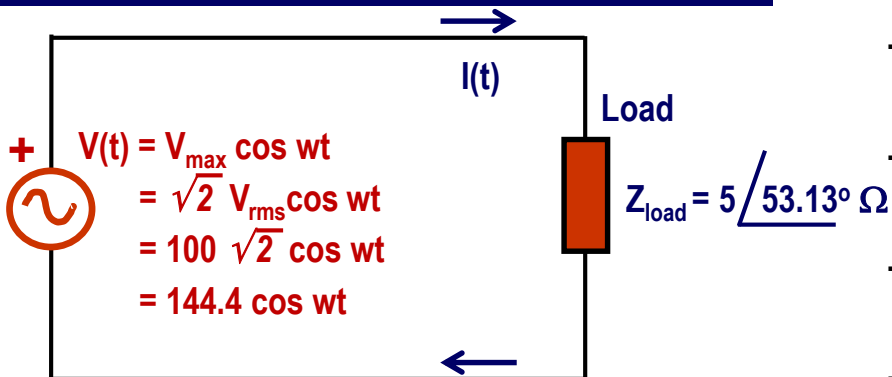
$$I_{rms} = I_{max} / \sqrt{2} = 28.8 / \sqrt{2} = 20 \text{ Amp}$$



Example

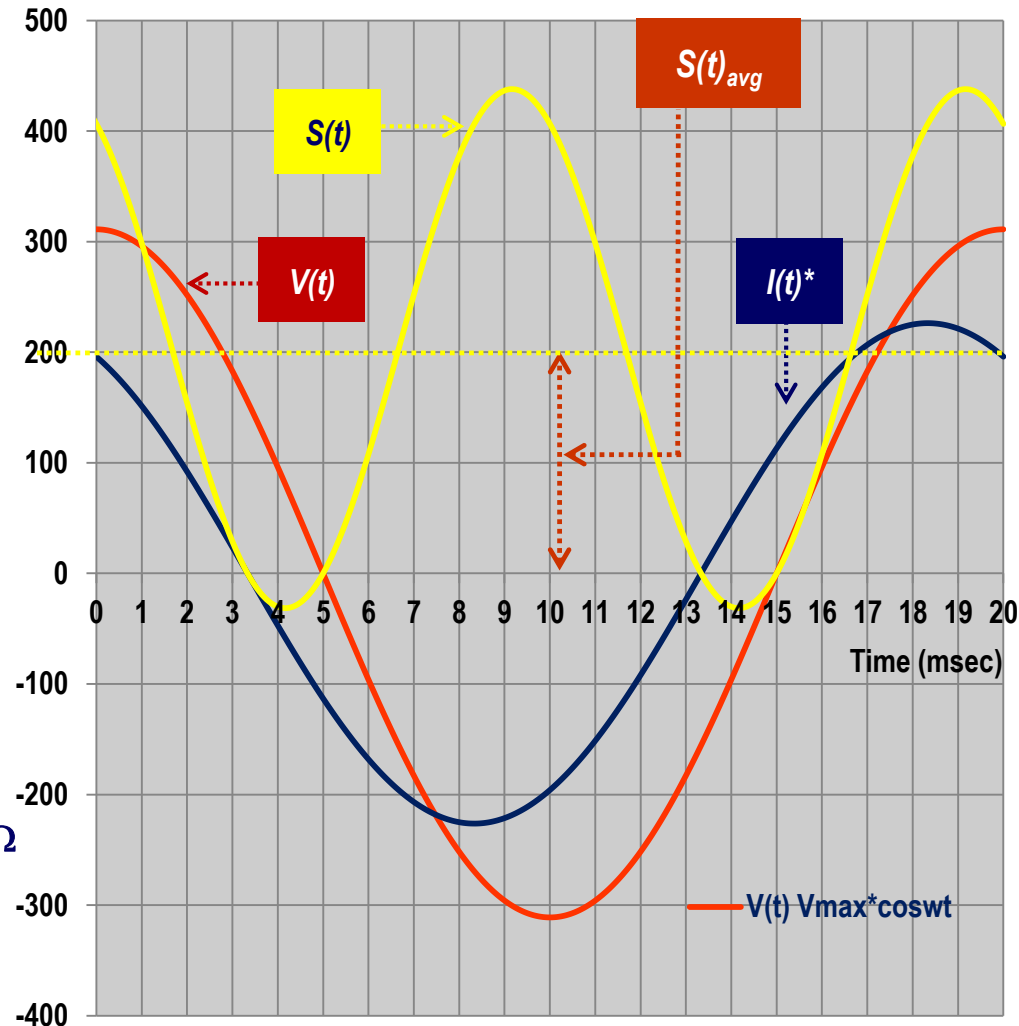

Example

Solution



$$S(t)_{avg} = V_{rms} I_{rms} \cos \theta$$

$$= 100 \times 20 \cos 53.13 = 1200 \text{ Watts}$$

$$S = V \times I^*$$

$$= \sqrt{2} \times 100 \cos wt \times \sqrt{2} \times 20 \cos (wt + 53.13^\circ)$$
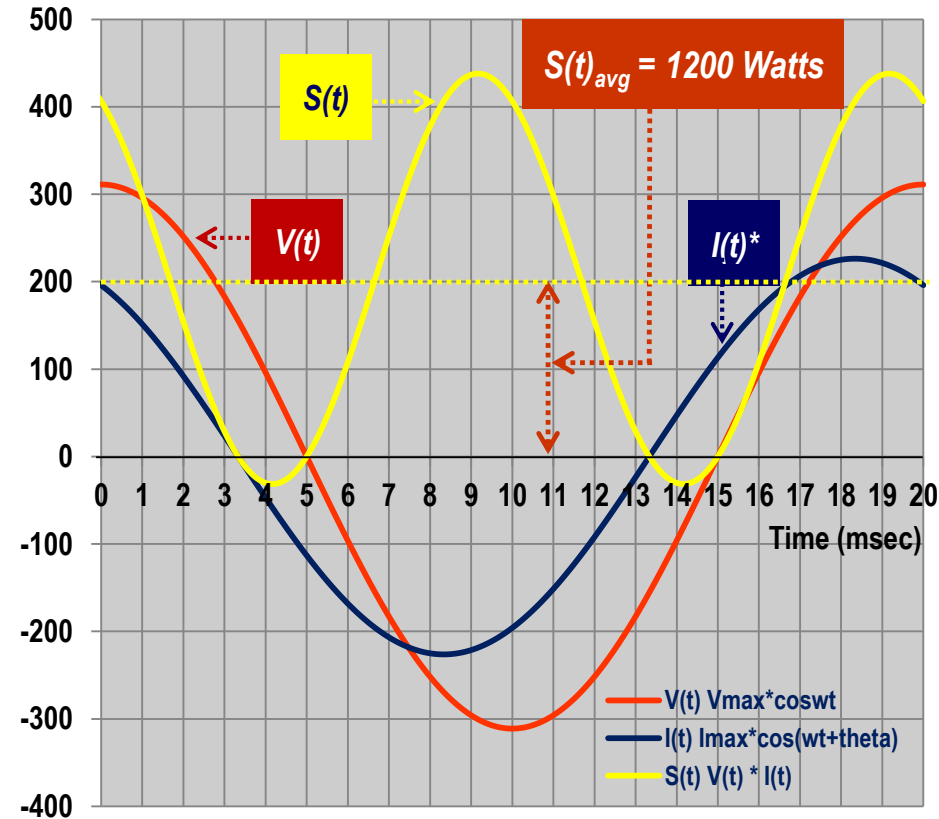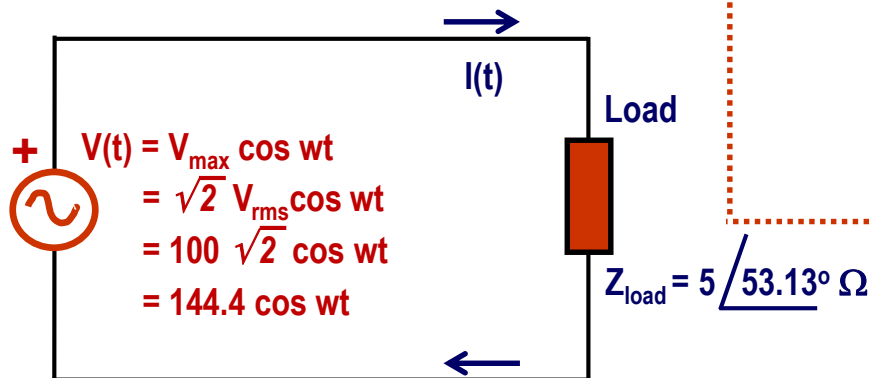
$$= 4000 \cos wt \times \cos (wt + 53.13^\circ)$$



Please note that;
 “-” sign here should be altered to “+” due to the
 conjugate operator in the definition of power:
 $S = V \times I^*$

Example



Solution

$$S(t) = 4000 \cos wt \times \cos (wt + 53.13^\circ)$$

or by using the following identity;

$$\cos a \cos b = \frac{1}{2} [\cos (a + b) + \cos (a - b)]$$
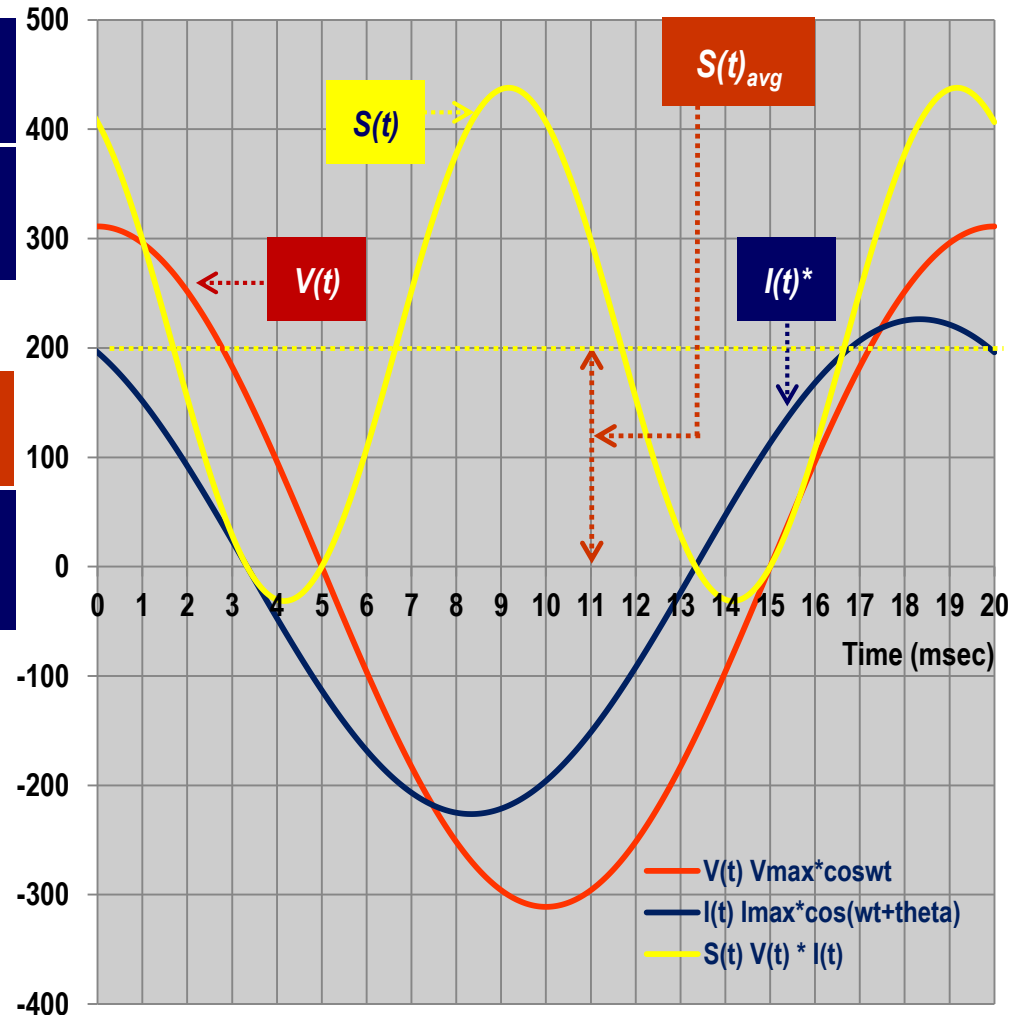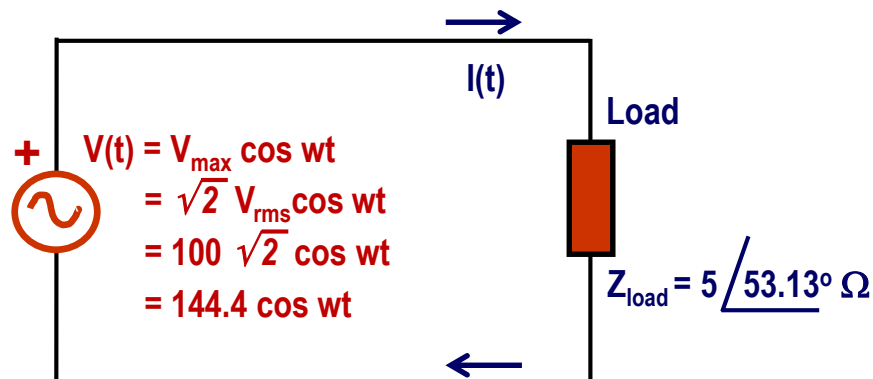
$$S(t) = 2000 [\cos (2wt + 53.13^\circ) + \cos 53.13^\circ]$$



Complex Power

Active Power Expression

Expanding the first term in the power expression;

$$S(t) = V_{rms} I_{rms} [\cos(2\omega t + \theta) + \cos \theta]$$

$$\cos(a + b) = \cos a \cos b - \sin a \sin b$$

Expanding the first term in the power expression;



$$S(t) = V_{rms} I_{rms} (\cos 2\omega t \cos \theta - \sin 2\omega t \sin \theta + \cos \theta)$$

and recombining the cosine terms;

$$= V_{rms} I_{rms} [\cos \theta (1 + \cos 2\omega t) - \sin 2\omega t \sin \theta]$$

$$P(t) = \text{Active power}$$

$$Q(t) = \text{Reactive power}$$

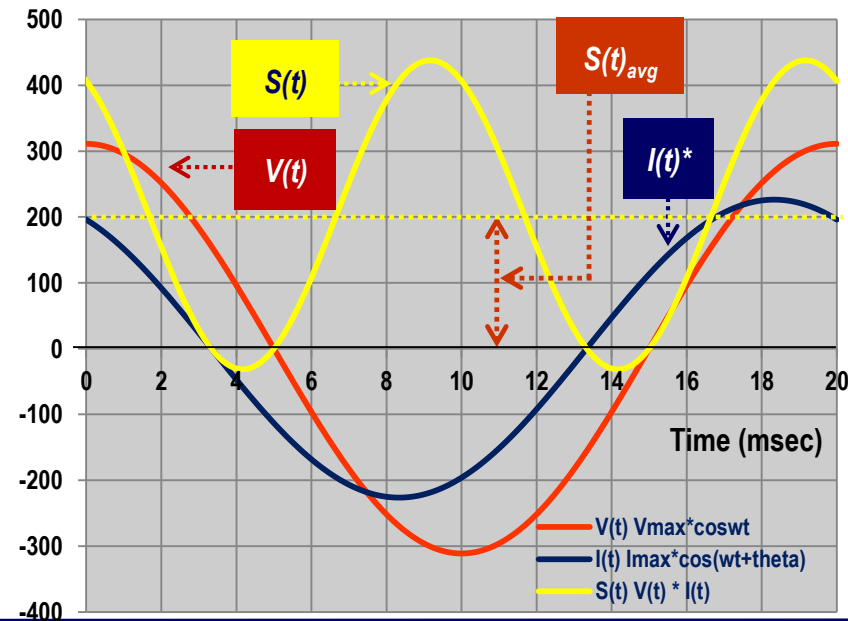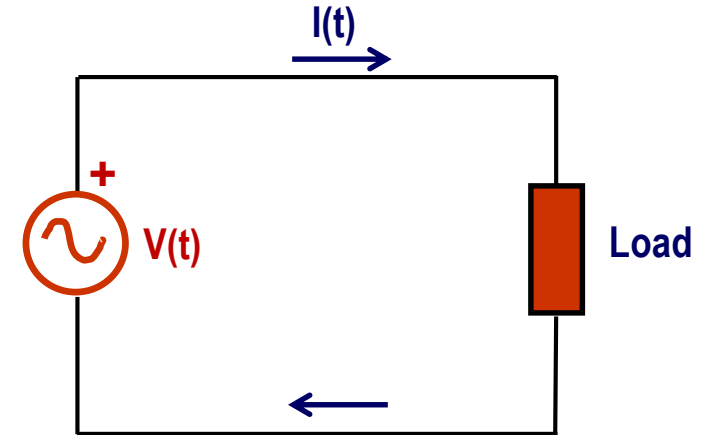


Complex Power

$$\begin{aligned}
 S(t) &= V_{rms} I_{rms} [\cos \theta (1 + \cos 2\omega t) - \sin 2\omega t \sin \theta] \\
 &= V_{rms} I_{rms} \cos \theta (1 + \cos 2\omega t) - \underbrace{V_{rms} I_{rms} \sin \theta}_{Q_{max}} \sin 2\omega t \\
 &= V_{rms} I_{rms} \cos \theta (1 + \cos 2\omega t) - Q_{max} \sin 2\omega t
 \end{aligned}$$

$P(t)$ = Active power
Please note that $P(t)$ is nonnegative

$Q(t)$ = Reactive power
Please note that $Q(t)$ has zero mean
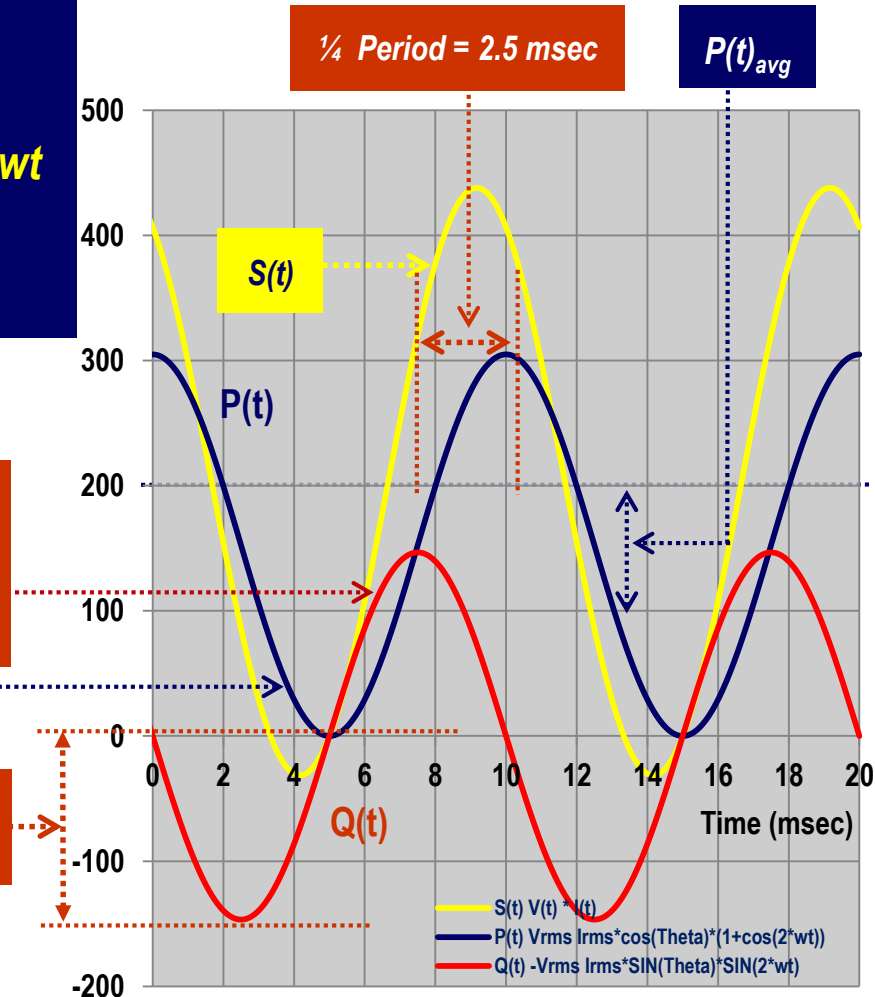
$$Q_{max} = V_{rms} I_{rms} \sin \theta$$



Active and Reactive Power Waveforms – Summary




$$S(t) = V_{rms} I_{rms} \cos \theta (1 + \cos 2\omega t) - V_{rms} I_{rms} \sin \theta \sin 2\omega t$$

Active power


$$P(t)_{avg} = V_{rms} I_{rms} \cos \theta$$

Reactive power

$$Q(t) = -Q_{max} \sin 2\omega t$$

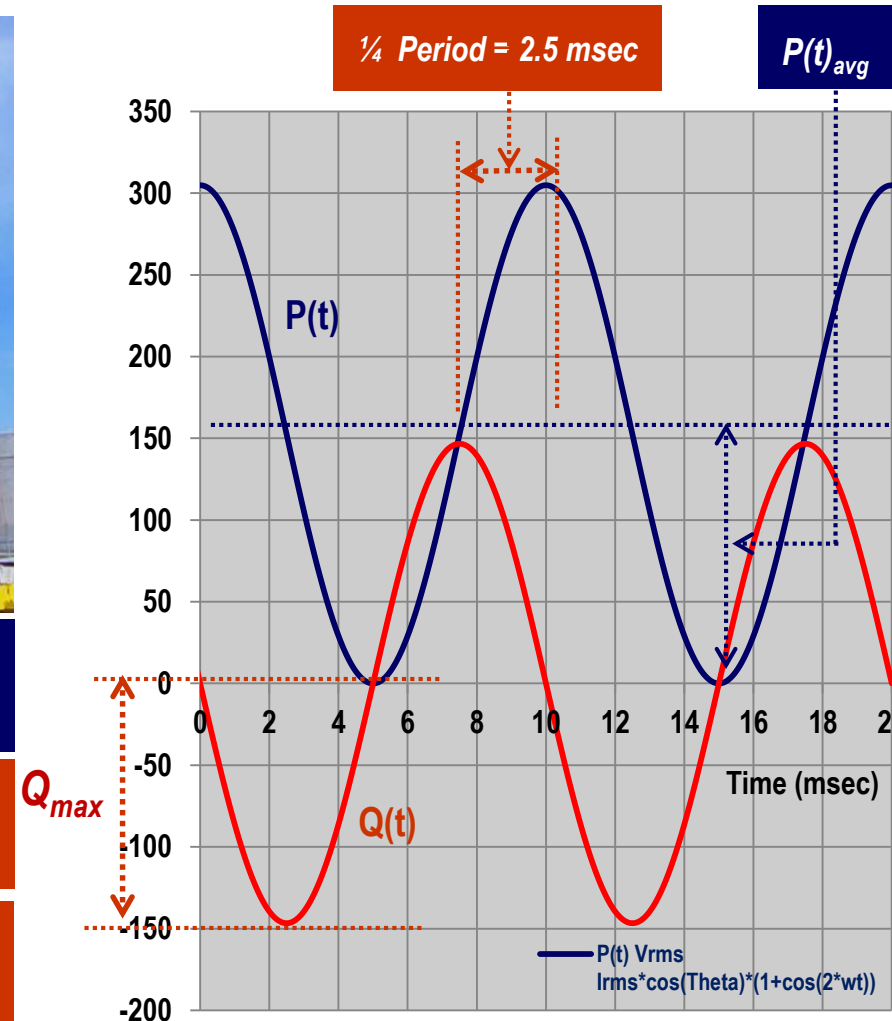

Active and Reactive Power Waveforms

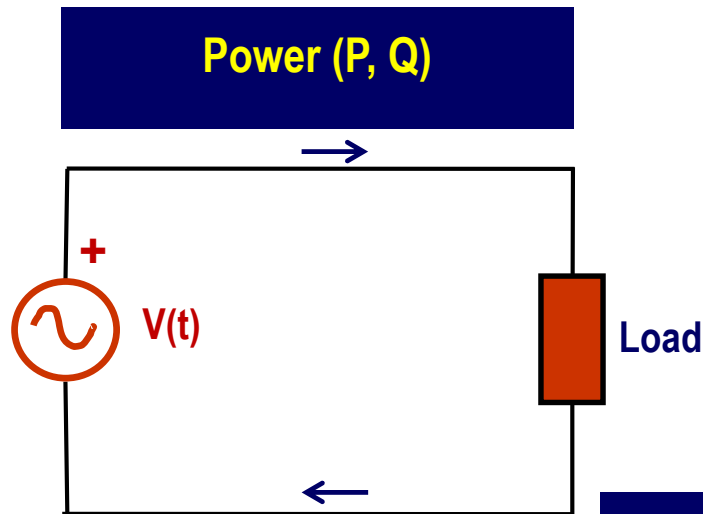


$P(t)$ = Active power

$Q(t)$ = Reactive power

One cycle \longleftrightarrow 10 msec

Hence,

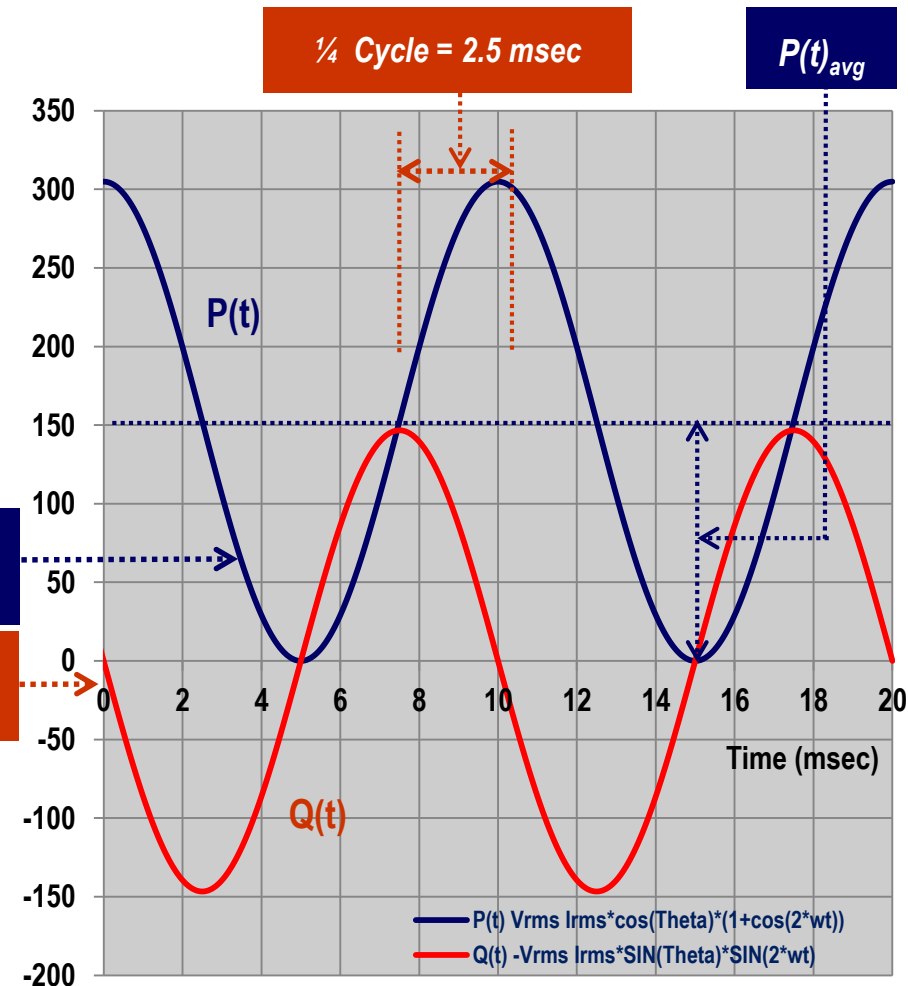
$1/4$ cycle = $360^\circ / 4 = 90^\circ \longleftrightarrow$ 2.5 msec



Active and Reactive Power Waveforms


One cycle \longleftrightarrow 10 msec
Hence,
 $1/4$ cycle = $360^\circ / 4 = 90^\circ \longleftrightarrow$ 2.5 msec

Please note that Q leads P by 90°

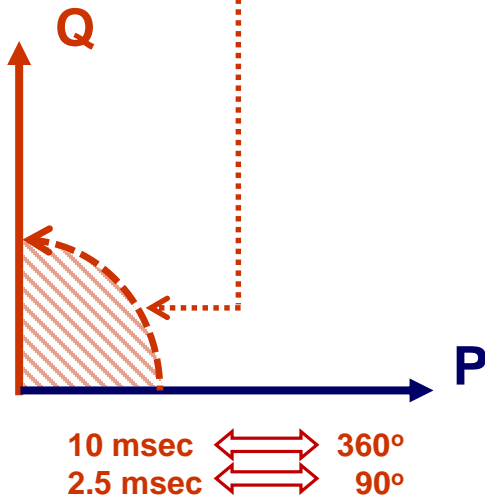

$P(t)$ = Active power

$Q(t)$ = Reactive power

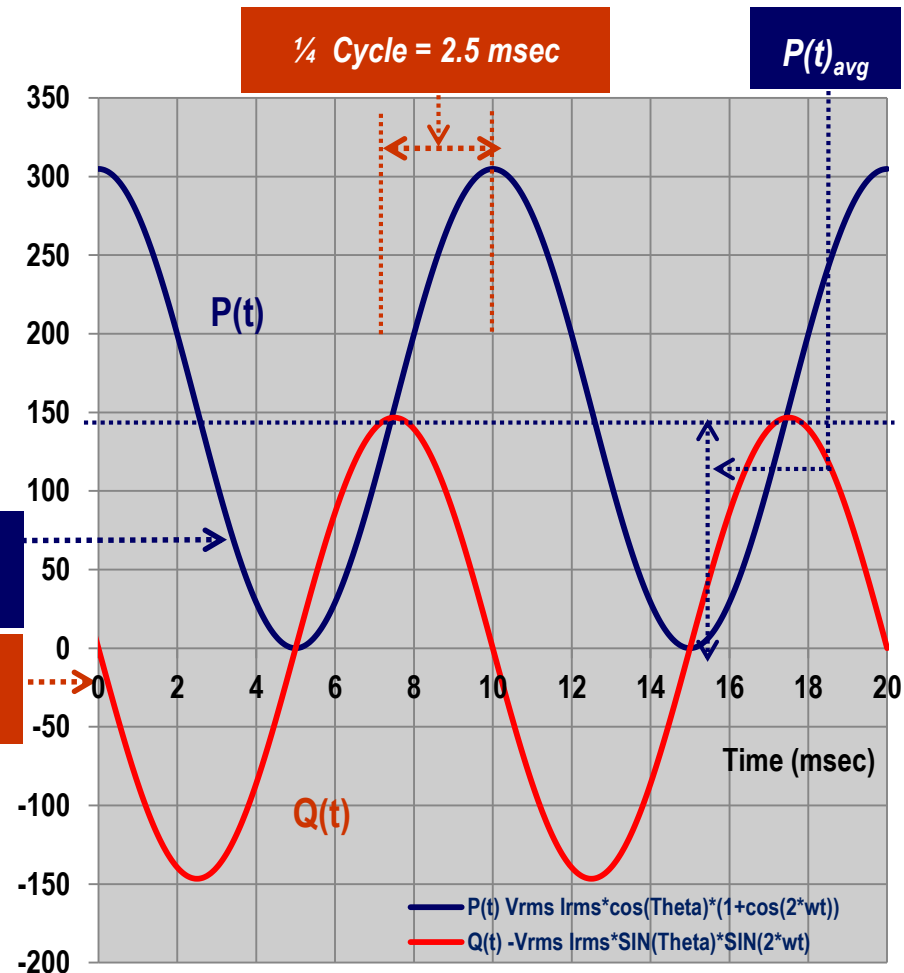

Active Power Waveform


$$P(t) = V_{rms} I_{rms} \cos \theta (1 + \cos 2\omega t)$$

$$= V_{rms} I_{rms} \cos \theta + V_{rms} I_{rms} \cos \theta \cos 2\omega t$$

$P(t)_{avg}$

$P(t)_{sinusoidal}$


Active Power (P)

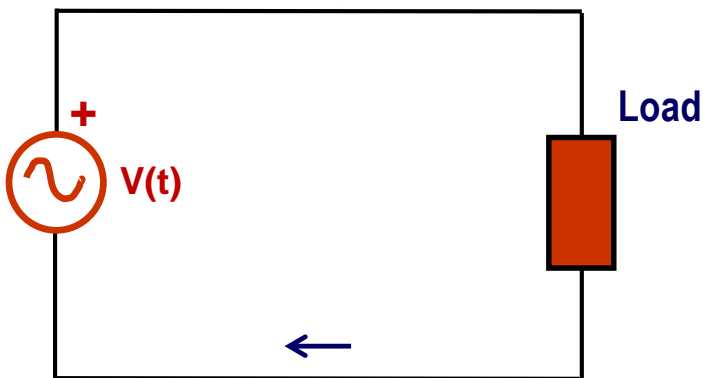

$$P(t)_{avg} = V_{rms} I_{rms} \cos \theta$$

$$= 150 \text{ W}$$

$P(t)$ = Active Power (Watt)

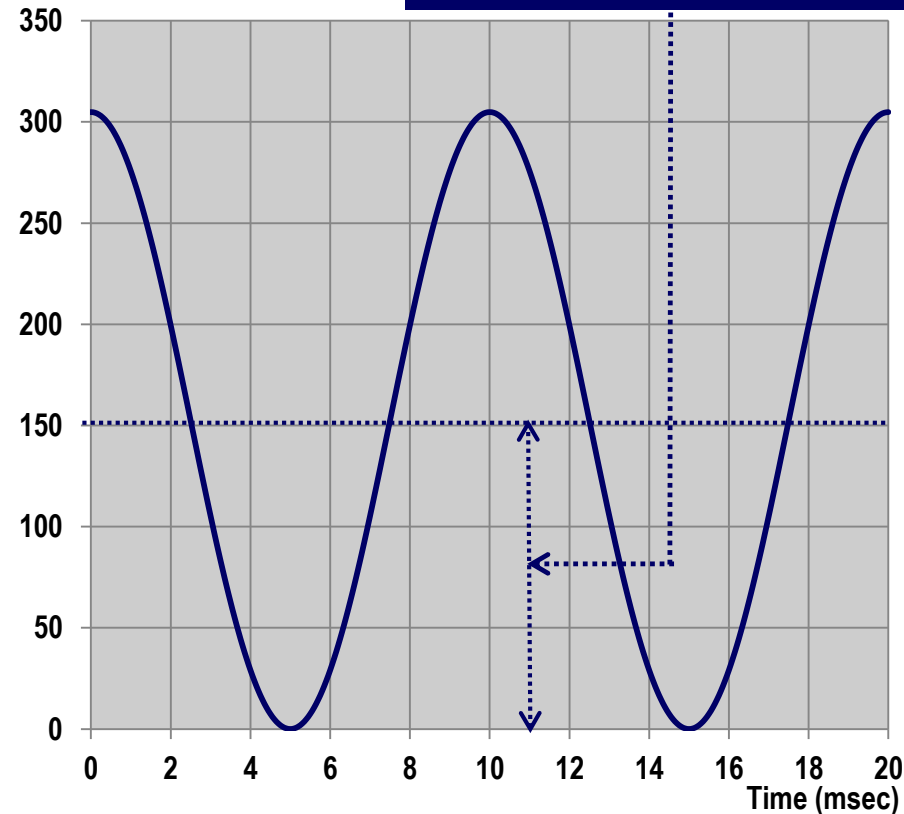

Reactive Power Waveform



$$Q(t) = -V_{rms} I_{rms} \sin\theta \times \sin 2\omega t$$

$$= -Q_{max} \sin 2\omega t$$


$Q(t)$ sinusoidal

Q_{max}


Reactive Power (Q)

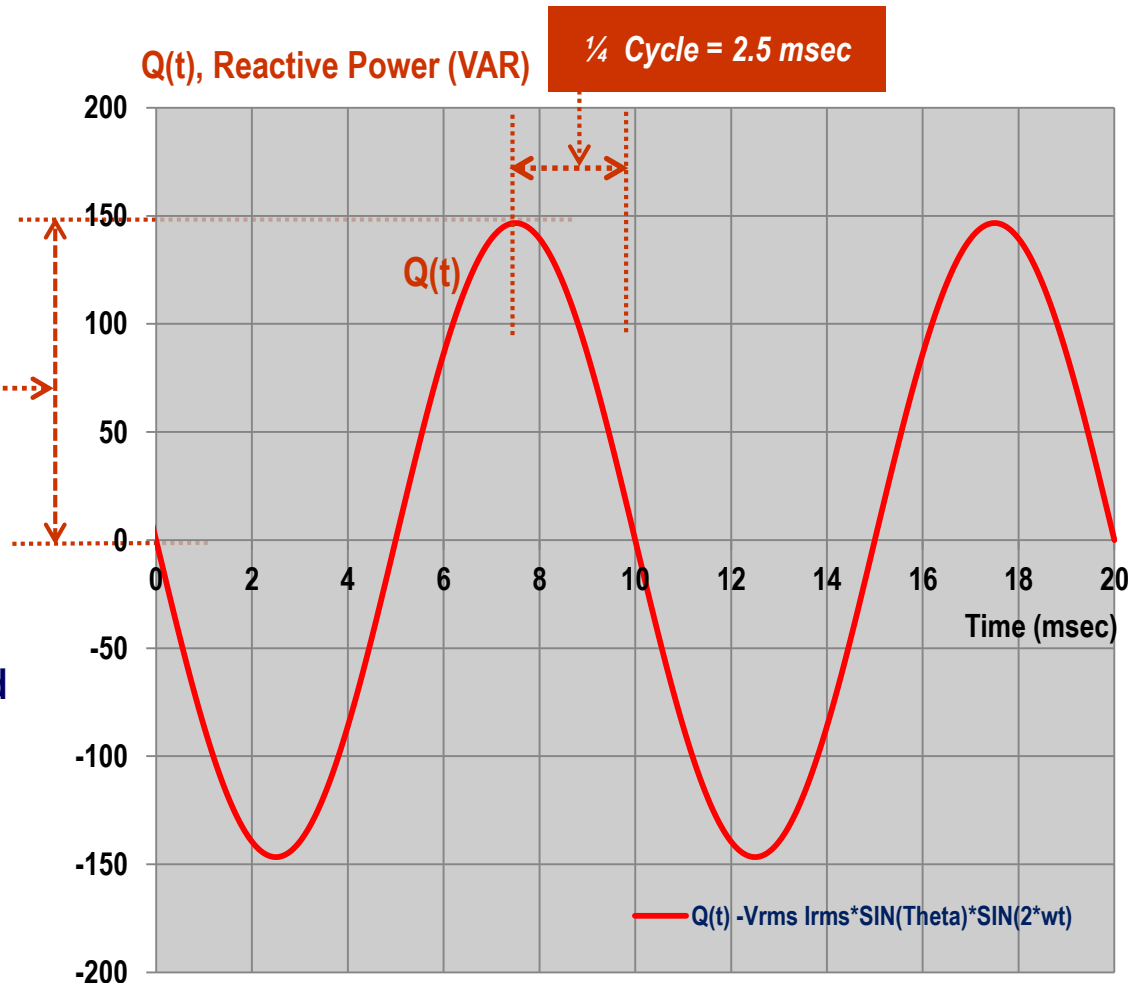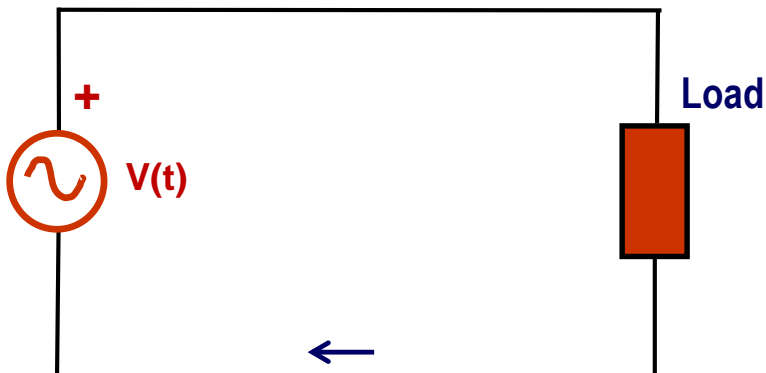

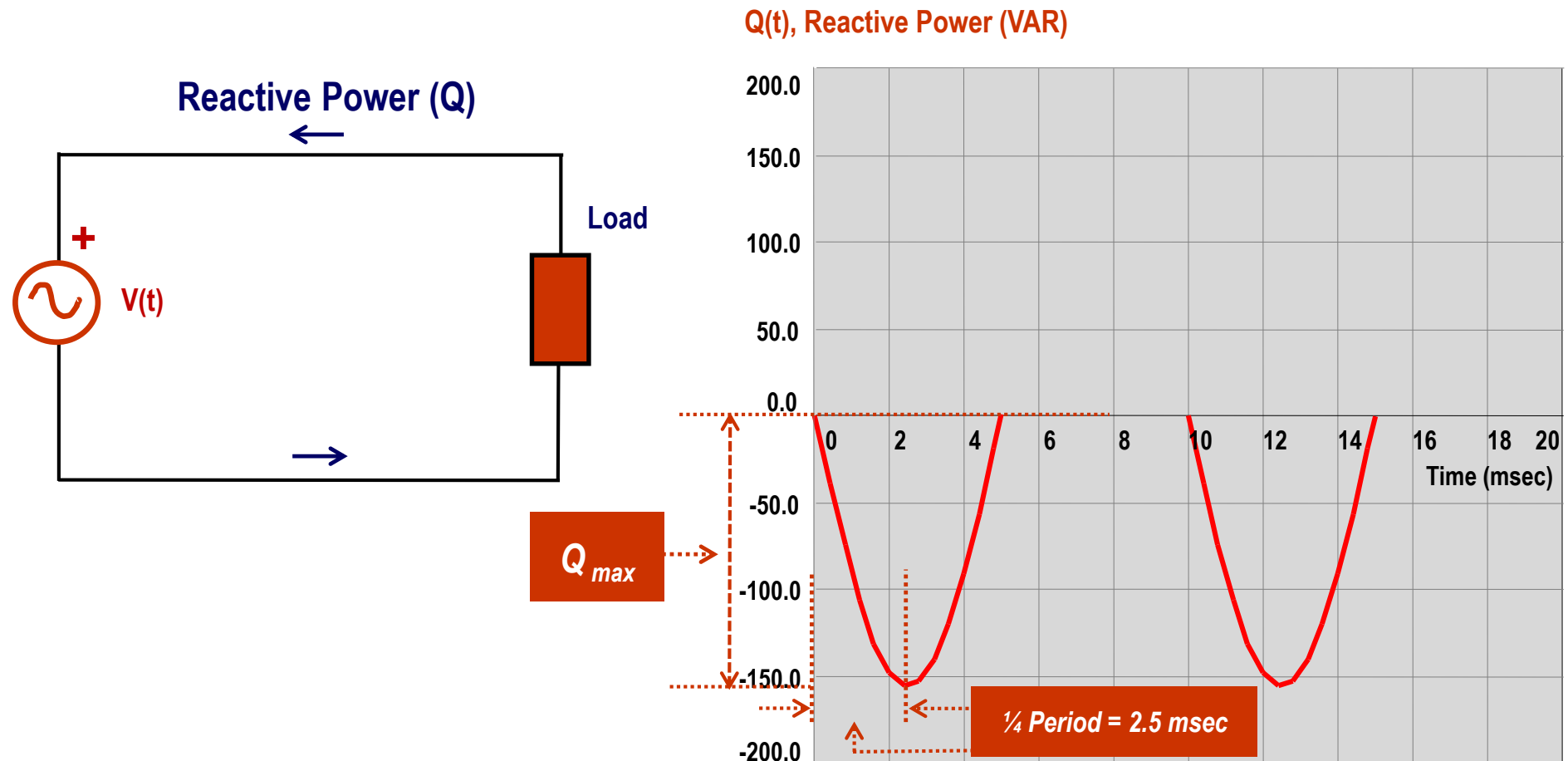Reactive Power Waveform (During the first 5 mseconds)



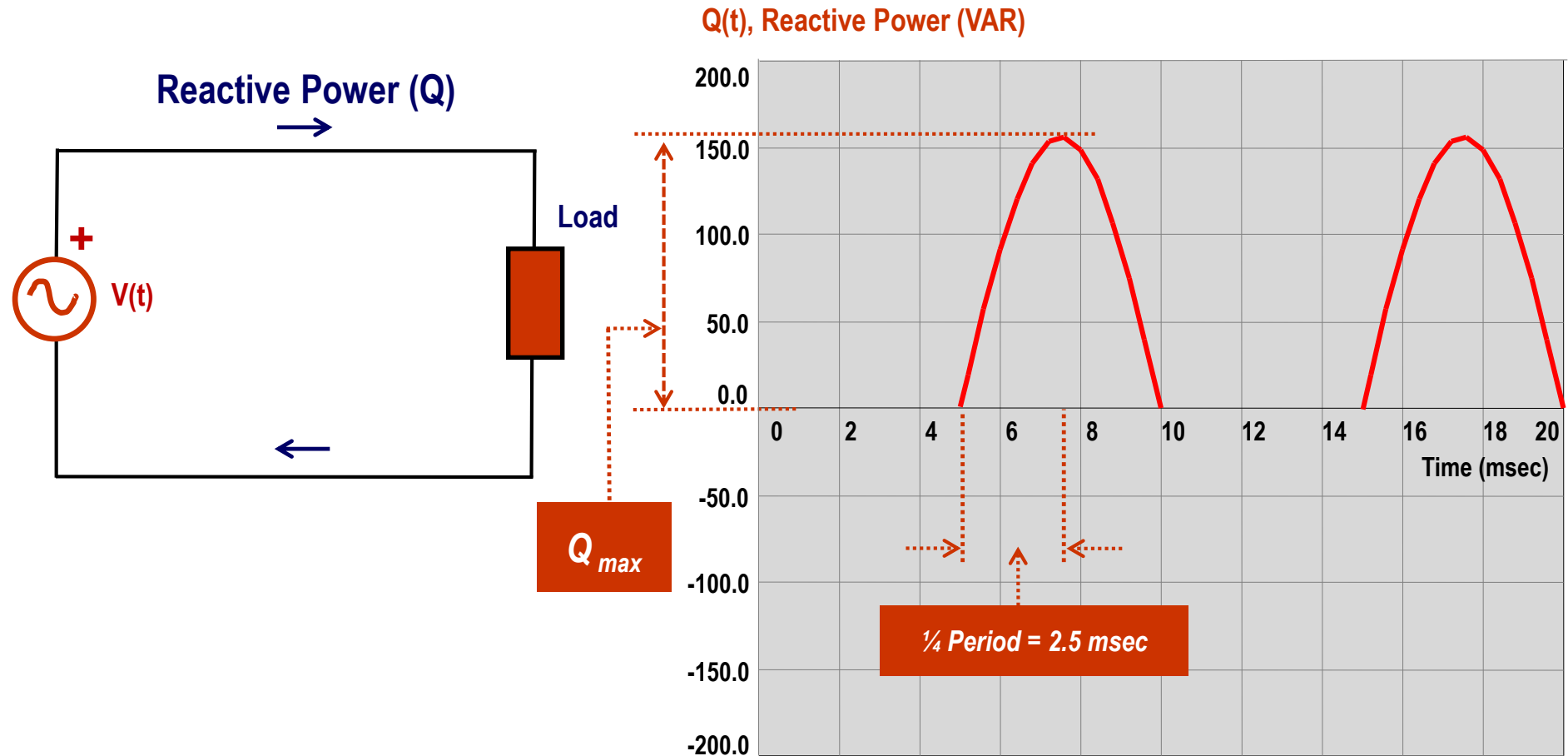Reactive Power Waveform (During the next 5 mseconds)




Active and Reactive Power Waveforms

Mean of $P(t)$ is called active power
Peak of $Q(t)$ is called reactive power


$$P(t)_{avg} = V_{rms} I_{rms} \cos \theta$$

$$Q_{max} = V_{rms} I_{rms} \sin \theta$$

$P(t)$ = Active Power (Watt)

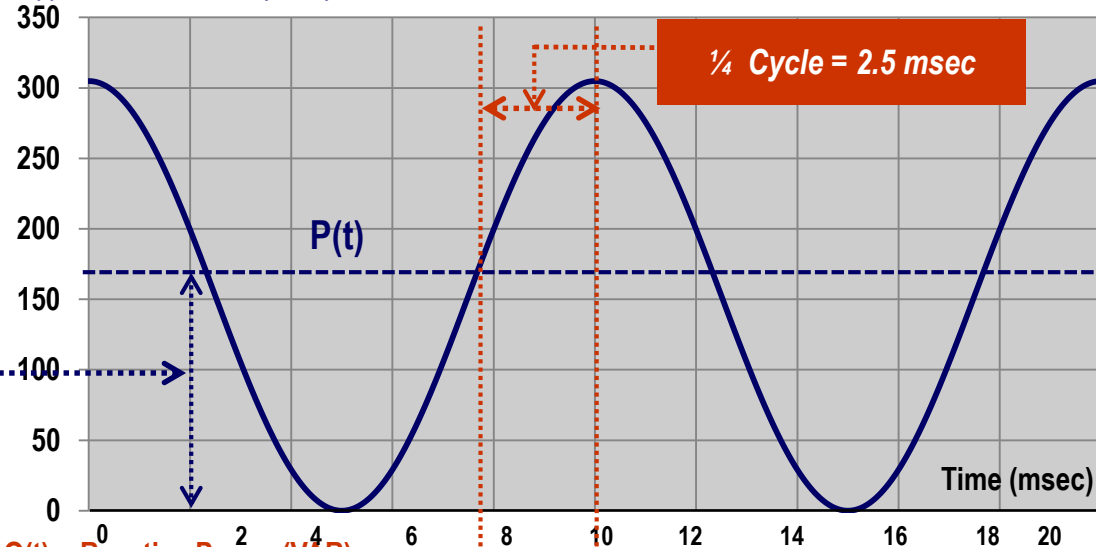

$Q(t)$ = Reactive Power (VAR)

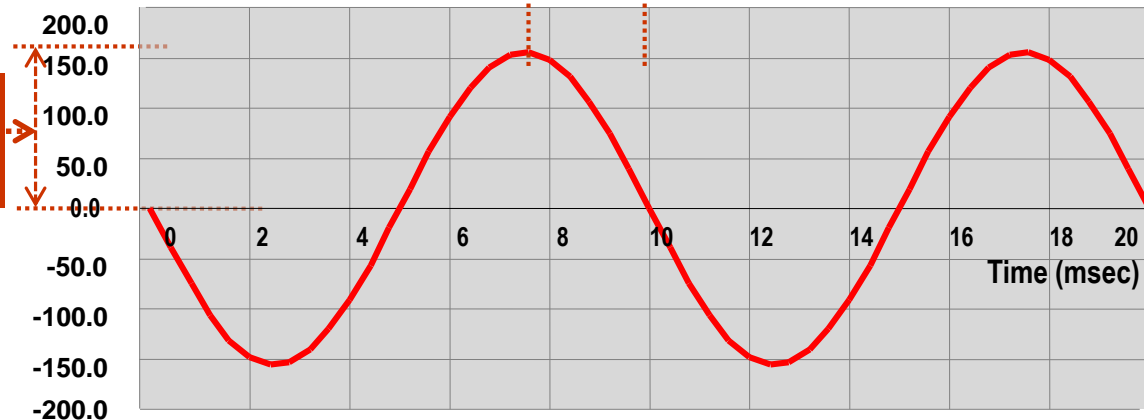

Period of Active and Reactive Power Waveforms

Period of Voltage and Current Waveforms


Angular speed: $\omega = 2\pi f$
 $= 2 \times 3.1415 \times 50 = 314 \text{ rad/sec}$

Time duration (period) of one revolution $= 1/f = 1/50$
 $= 0.020 \text{ sec} = 20 \text{ msec}$

Hence,

Angle for $\frac{1}{4}$ revolution $= 360^\circ / 4 = 90^\circ$
 Time duration (period) of $\frac{1}{4}$ revolution $= 20 \text{ msec} / 4$
 $= 5 \text{ msec}$

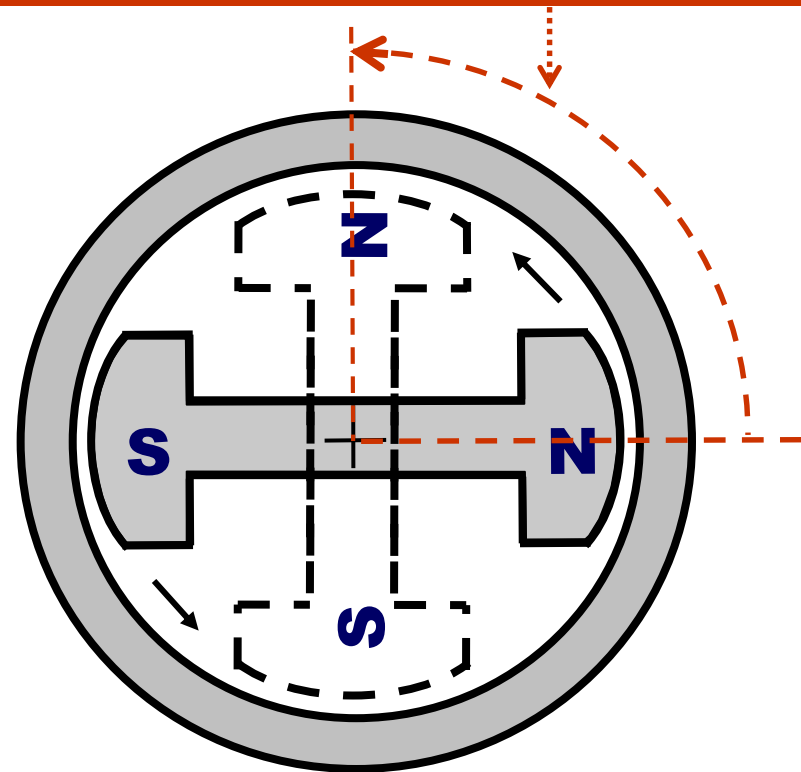Angle $= 90^\circ$,
 Time duration (Period) of $\frac{1}{4}$ revolution $= 20/4 \text{ sec}$
 $= 5 \text{ msec}$



Period of Active and Reactive Power Waveforms

Period of Active and Reactive Power Waveforms

Angular speed: $w' = 2 w = 4\pi f$
 $= 2 \times 31415 = 628 \text{ rad/sec}$


Hence,

Time duration (period) of one revolution = 10 msec
 Time duration (period) of $\frac{1}{4}$ revolution = $10 \text{ msec} / 4$
 $= 2.5 \text{ msec}$



Conclusion;

Time duration (period) of active and reactive power waveforms is half of those of voltage and current

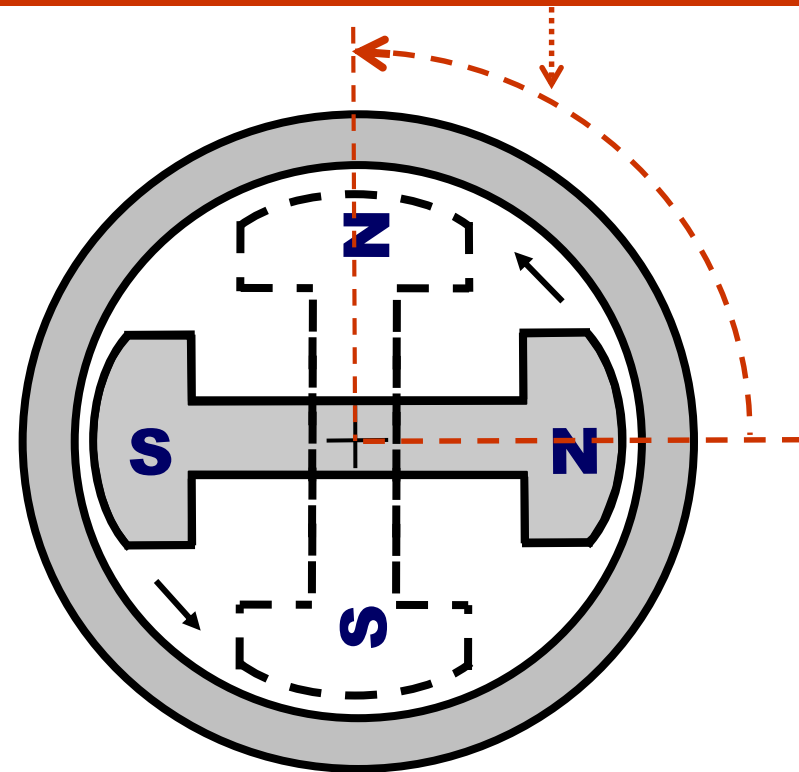Angle = 90° ,
 Time duration (Period) of $\frac{1}{4}$ revolution = $20/4 \text{ sec}$
 $= 5 \text{ msec}$



Active and Reactive Power Phasors

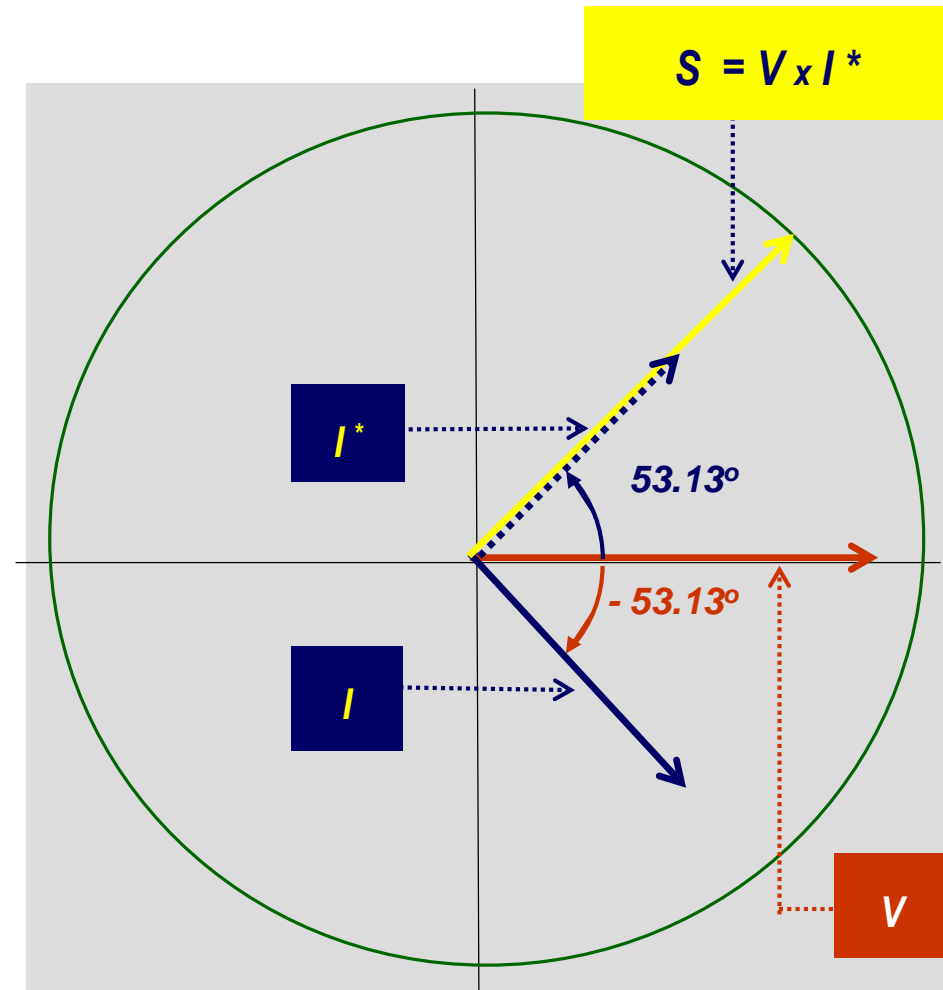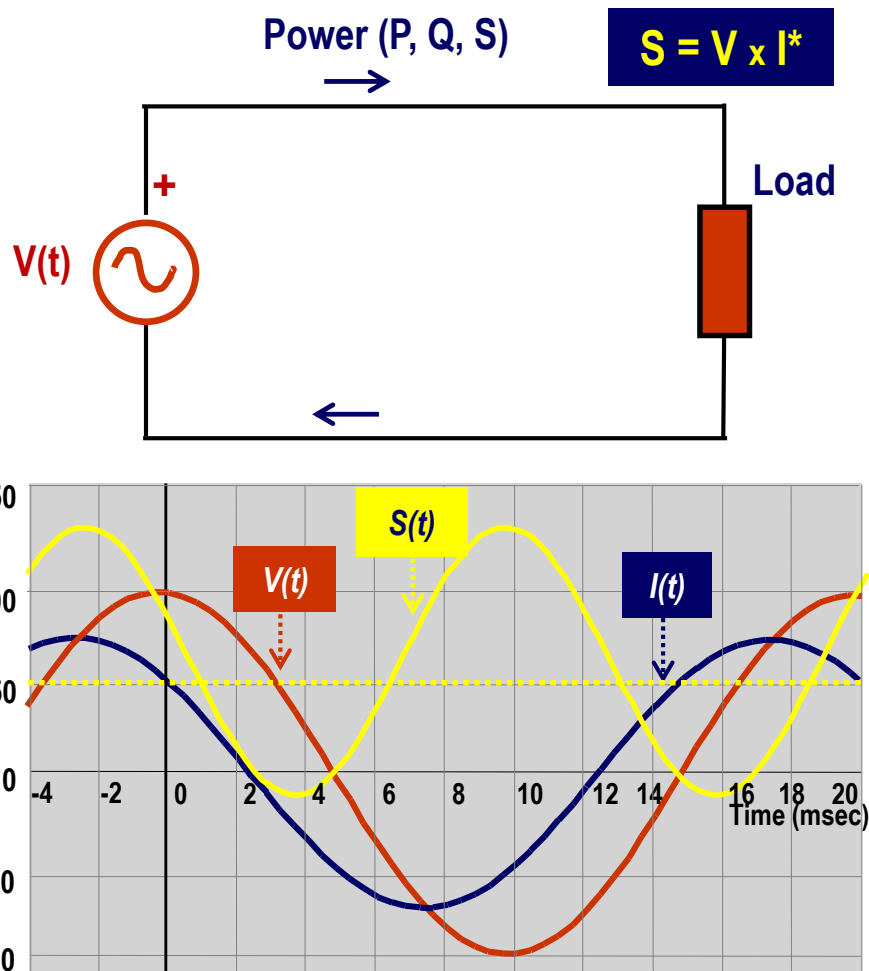

Active and Reactive Power Phasors

Total power

$$|S| = V_{rms} I_{rms}$$

$$|S| = \sqrt{P^2 + Q^2}$$

Active power



$$P_{avg} = V_{rms} I_{rms} \cos \theta$$

Reactive power

$$Q_{max} = V_{rms} I_{rms} \sin \theta$$

Power (P, Q, S)

$$S = V \times I^*$$

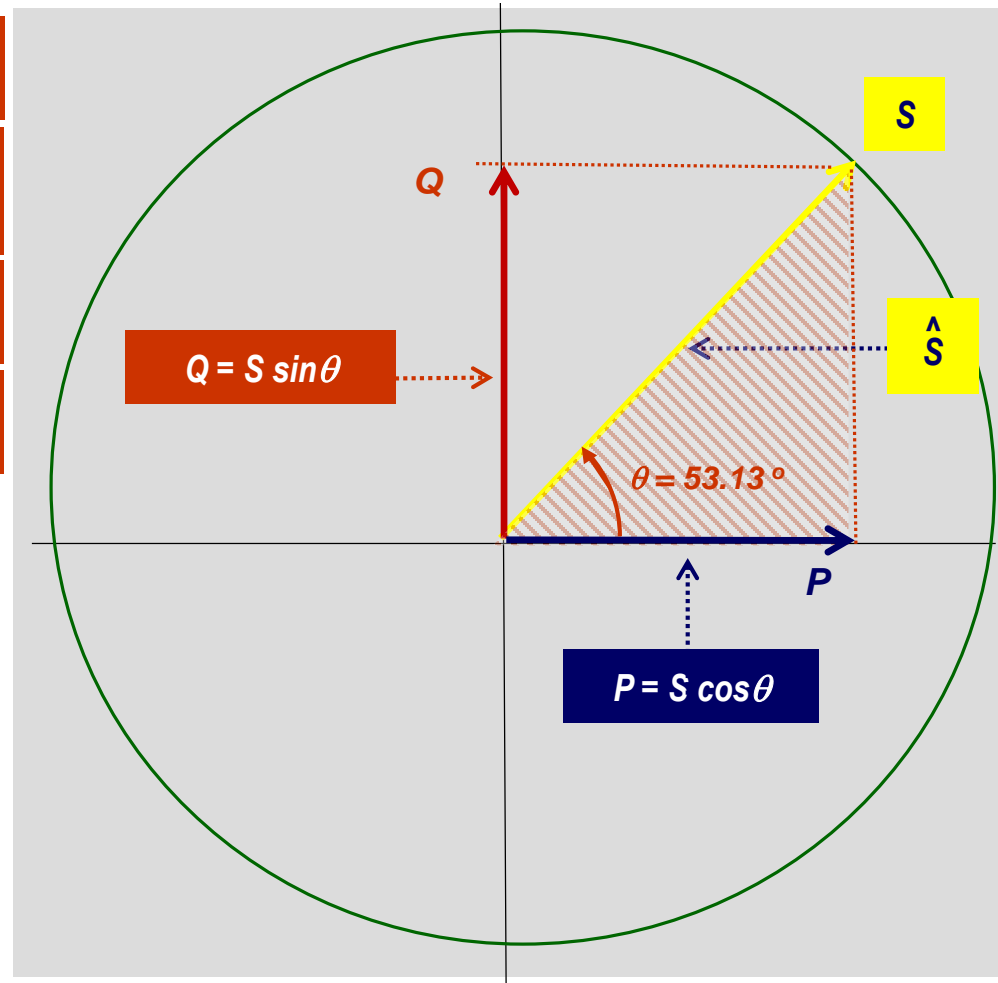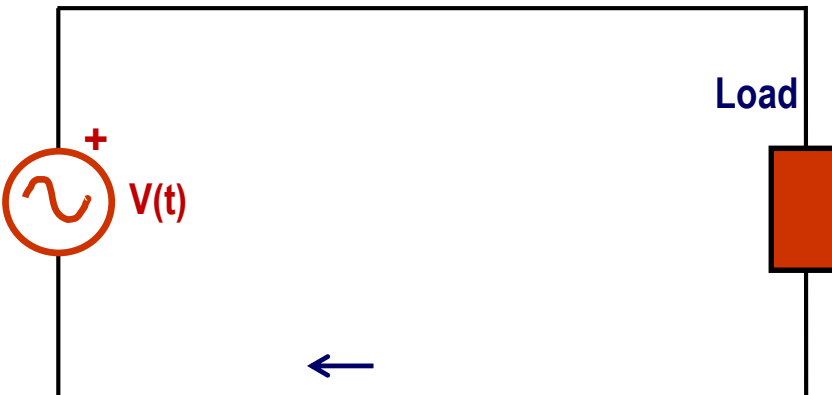

Active and Reactive Power Phasors

S - Total power

(k) VA (kVA)

P - Active power

(k) Watt (kW)


Q - Reactive power

(k) VAR (kVAR)

Please note that this angle is dependent only on the resistance R and reactance X of the load, i.e.

$$\theta = \tan^{-1} X / R$$

$$= \tan^{-1} Q / P$$

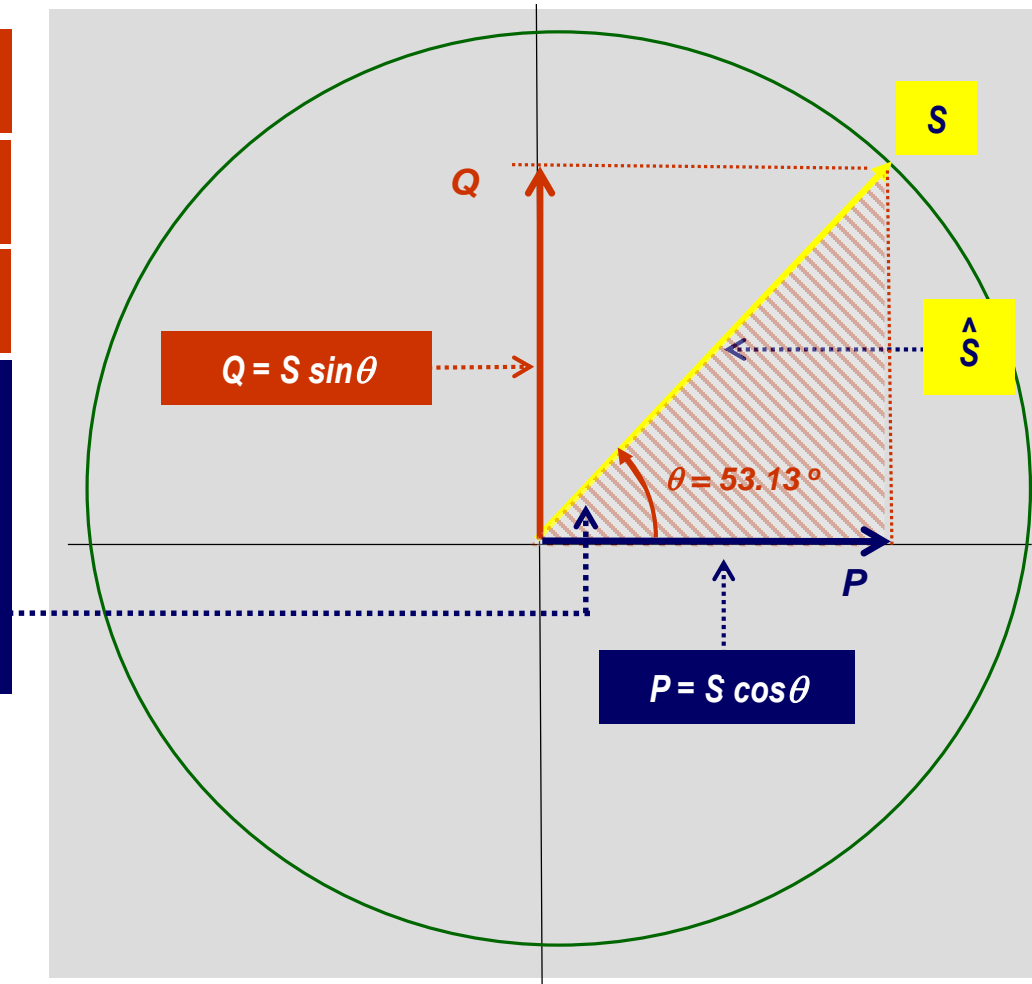

Basic Conversions

Polar Representation

$$S \angle \theta$$

Please note that this angle is dependent only on the resistance R and reactance X of the load

$$\theta = \tan^{-1} X / R$$

$$= \tan^{-1} Q / P$$

$$X / R = Q / P$$


i.e. if $X = 0 \rightarrow Q = 0$

$$P = S \cos \theta, \quad Q = S \sin \theta$$


$$S = \sqrt{P^2 + Q^2}, \quad \theta = \tan^{-1} (Q / P)$$

Rectangular Representation


$$P + j Q$$

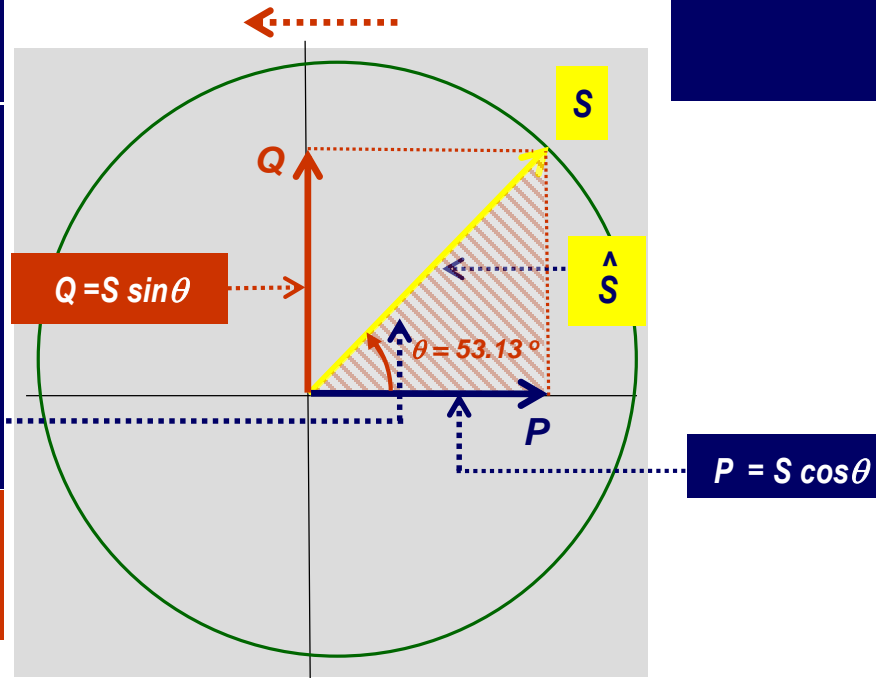

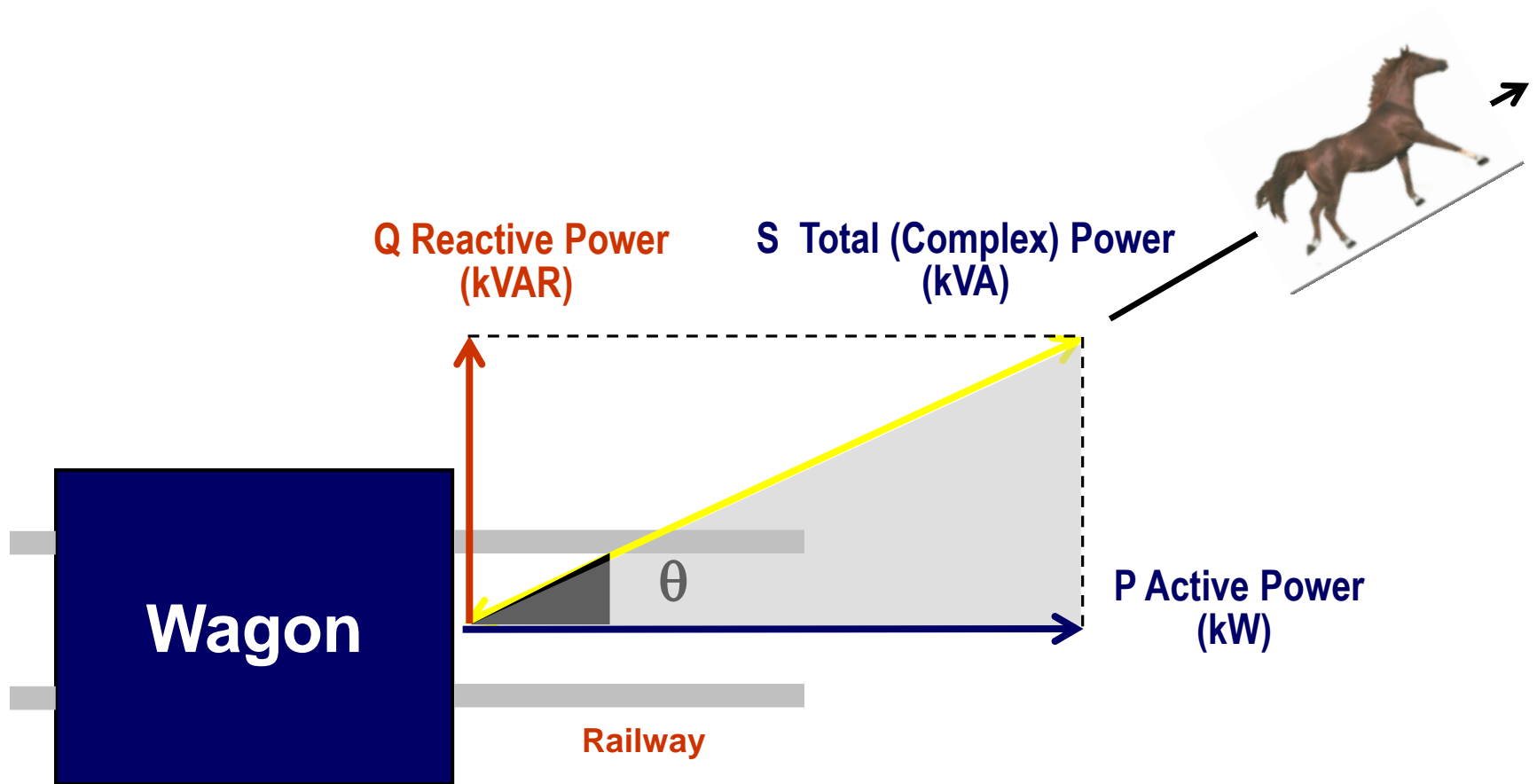
Active and Reactive Powers (in the first 5 mseconds)




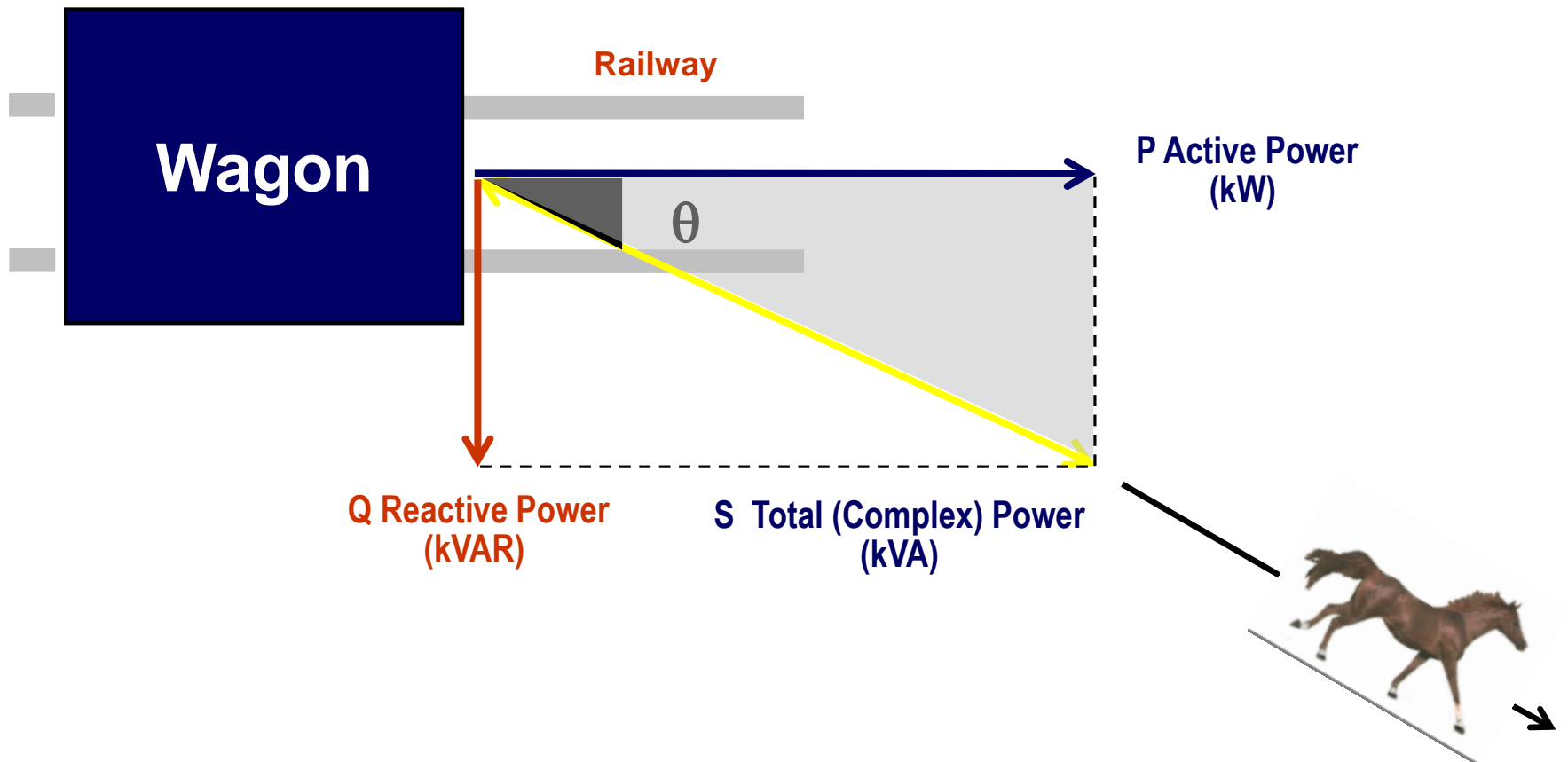
Active and Reactive Powers (in the next 5 mseconds)



Active and Reactive Powers

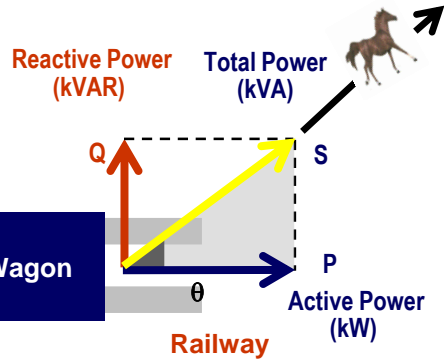

Q Reactive Power (kVAR)

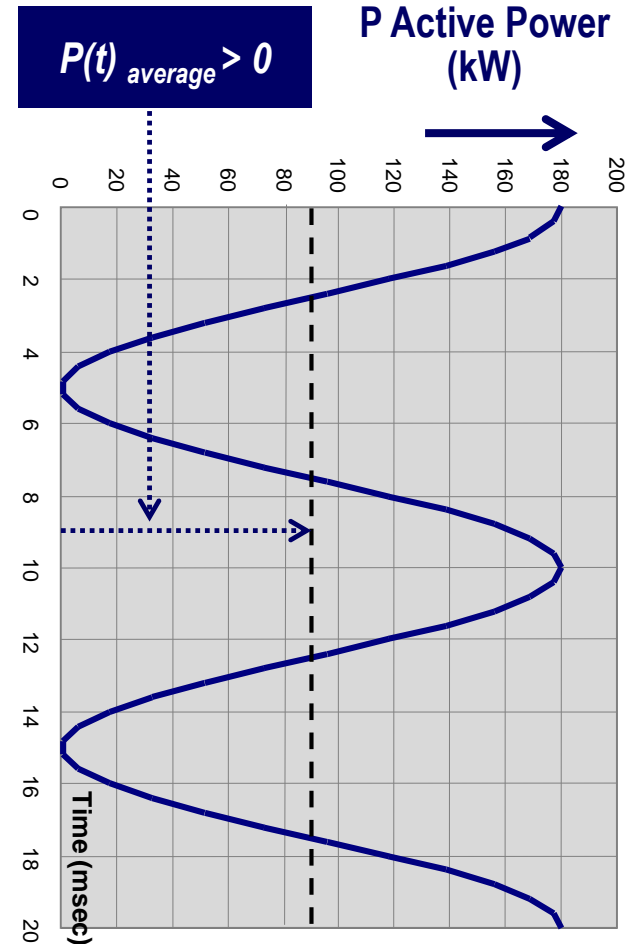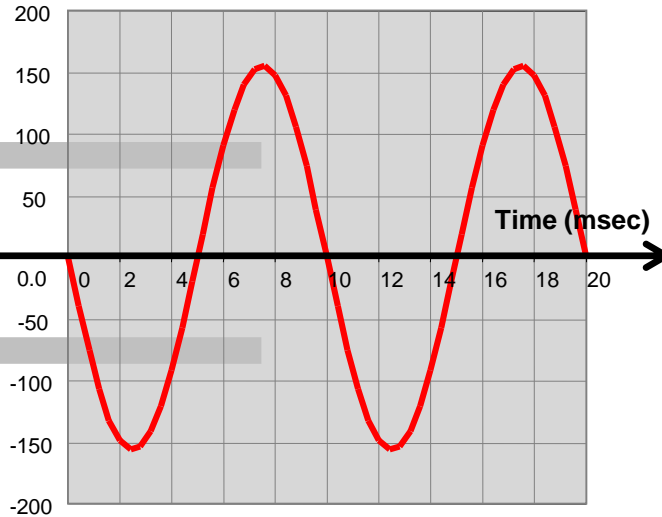

Active and Reactive Powers

Polar Representation


$$S \angle \theta$$

$$P = S \cos \theta, \quad Q = S \sin \theta$$

$$S = \sqrt{P^2 + Q^2}, \quad \theta = \tan^{-1}(Q / P)$$

Rectangular Representation

$$P + jQ$$

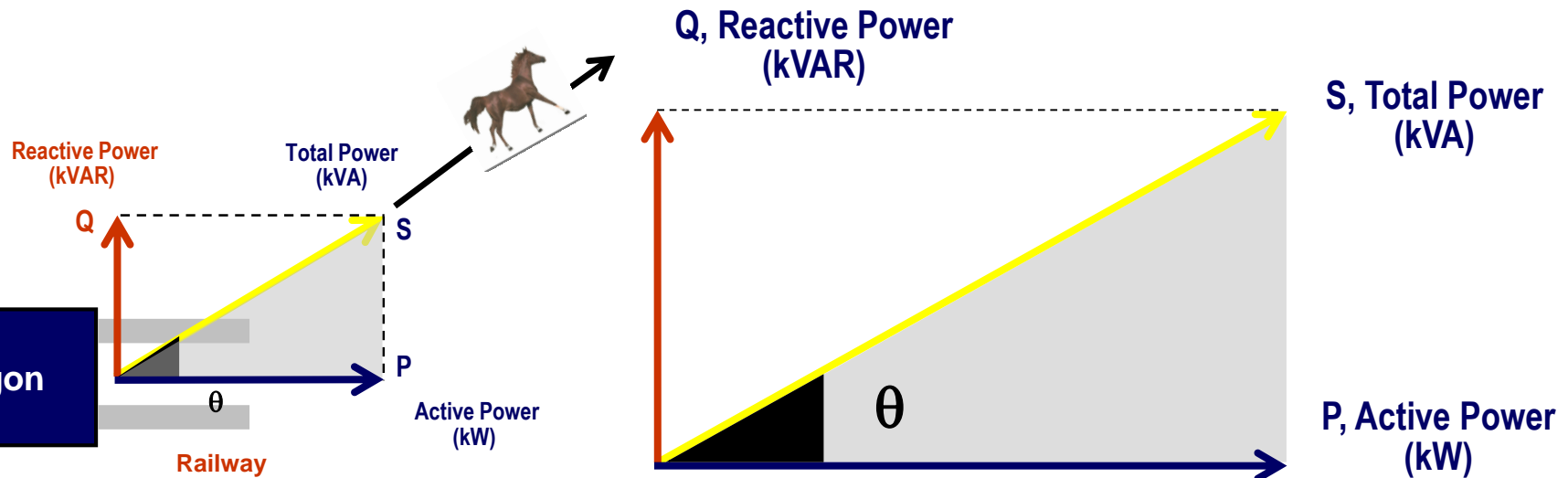

Active and Reactive Powers

Total power

$$|S| = V_{rms} I_{rms}$$

$$|S| = \sqrt{P^2 + Q^2}$$

Active power


$$|P| = V_{rms} I_{rms} \cos \theta$$

Reactive power

$$|Q| = V_{rms} I_{rms} \sin \theta$$



Q, Reactive Power
(kVAR)

S, Total (Complex) Power
(kVA)

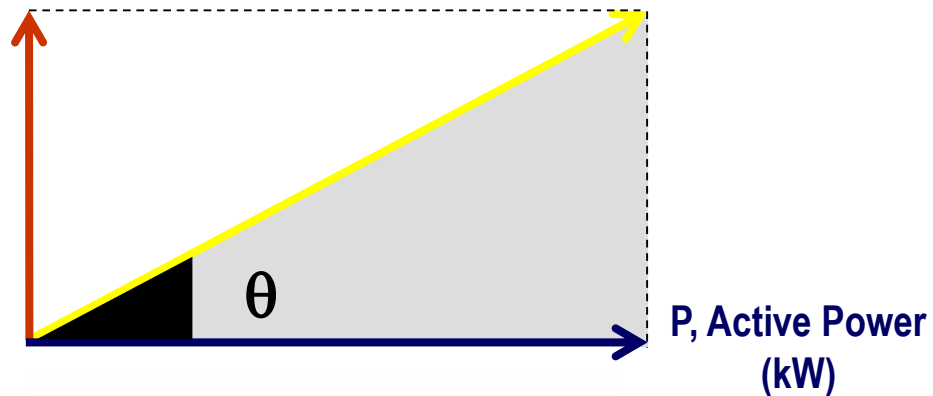

Reactive Power
(kVAR)

Total Power
(kVA)

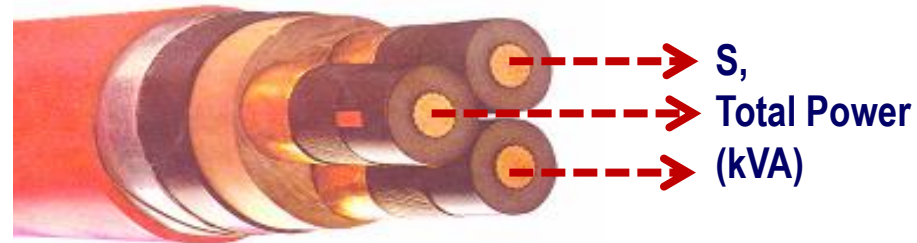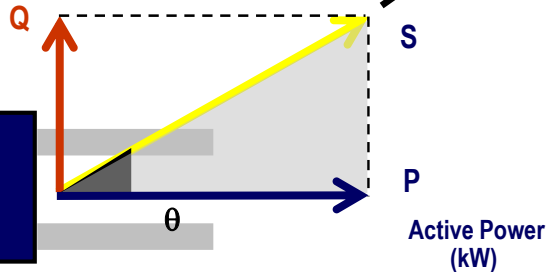

AC Power

Power Meters

Analog



Digital



Power Analyzer





Clamp Type Current Transformers

Reactive Power Compensation

Definition


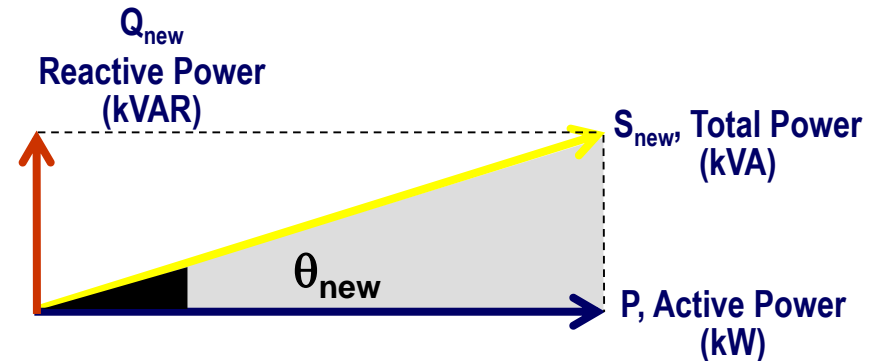
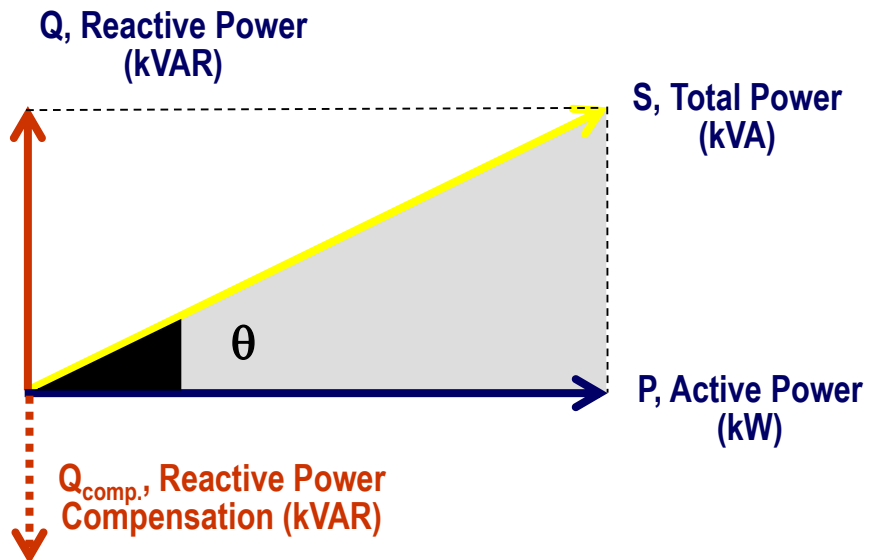
Reactive power compensation is partial or full cancellation of the reactive component of complex power by introducing a negative (compensation) component



Reactive Power Compensation

How is it Realized ?

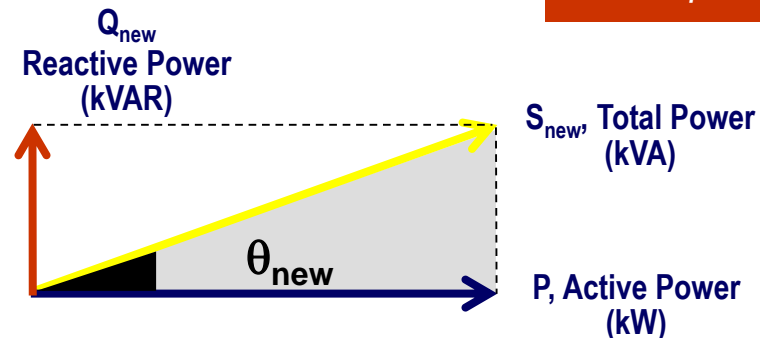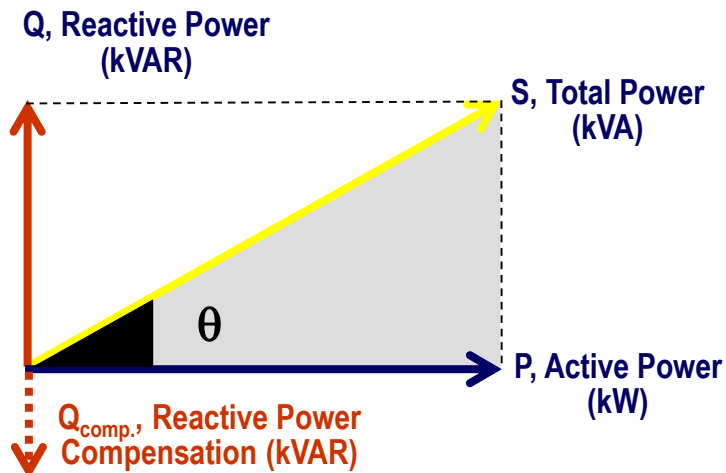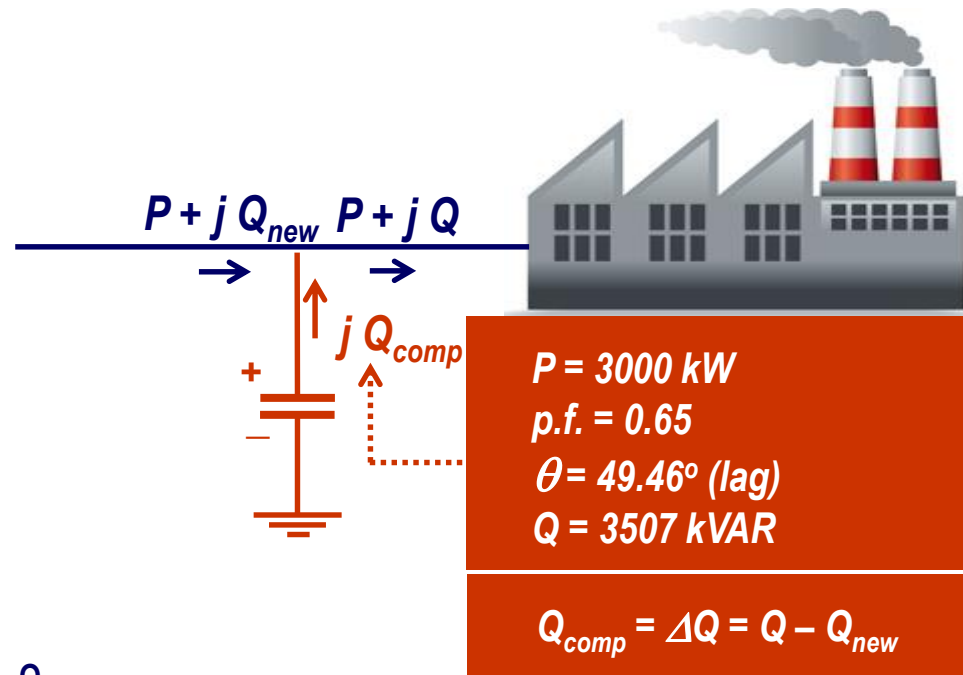Reactive power compensation is realized by connecting a capacitor bank in parallel with the load, satisfying the reactive power need of the load.



Power Factor

Definition


Cosine of the angle between S and P is called **Power Factor** of the load

$$\text{Power Factor} = p.f. = \cos \theta$$


$$= \cos (\tan^{-1} Q / P)$$

Please note that reducing Q means reducing the angle θ , and hence increasing power factor

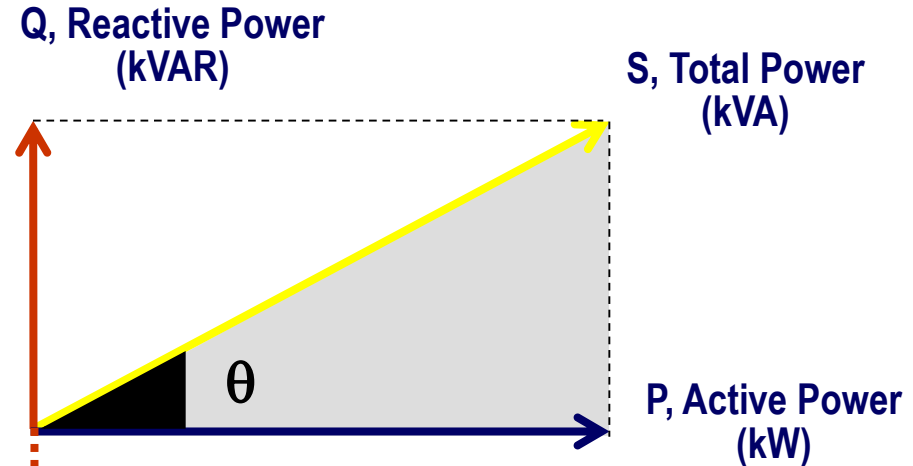Hence, reactive power compensation is sometimes called as “**Power Factor Correction**”, i.e. correcting power factor to a value, near unity



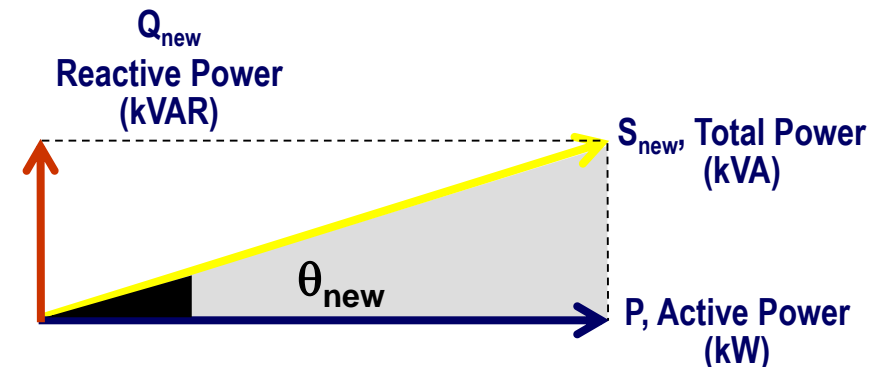$Q_{comp.}$, Reactive Power Compensation (kVAR)




Full or Partial Compensation

Full Compensation

Full compensation is the case, where Power Factor is unity
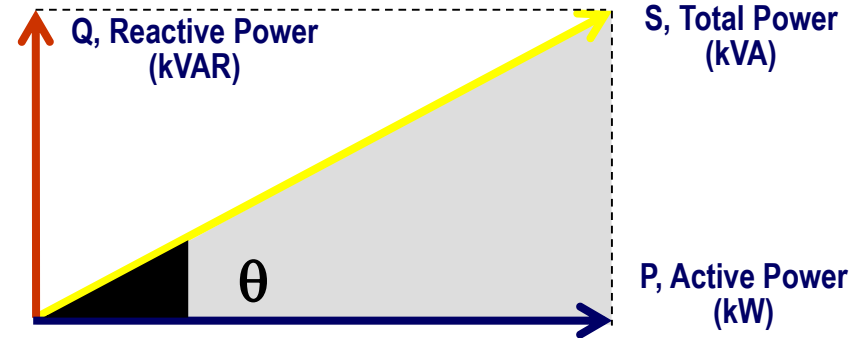
$$\begin{aligned} \text{Power Factor}_{\text{new}} &= p.f._{\text{new}} = \cos \theta_{\text{new}} \\ &= \cos (\tan^{-1} 0 / P) = 1 \end{aligned}$$



Full Compensation


$$Q_{\text{new}} = 0 \quad \theta_{\text{new}} = 0 \quad S_{\text{new}} = P$$



Partial Compensation

Partial compensation is the case, where Power Factor is raised to a level below unity
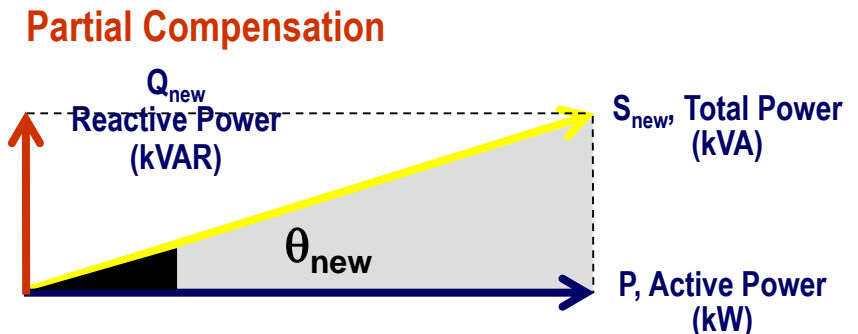
$$\begin{aligned} \text{Power Factor}_{\text{new}} &= p.f._{\text{new}} = \cos \theta_{\text{new}} \\ &= \cos (\tan^{-1} Q_{\text{new}} / P) \end{aligned}$$



Partial Compensation

Charging Principle Applied by TEDAS

If

$$|Q/P| > 1/3$$

Then, reactive power is charged

If

$$|Q/P| < 1/3$$

Then, reactive power is free

Please note that


$$|Q/P| > 1/3$$

means;

$$\tan^{-1}(1/3) = 18.435^\circ$$

$$\cos 18.435^\circ = 0.949 \approx 0.95$$

Q, Reactive Power
(kVAR)

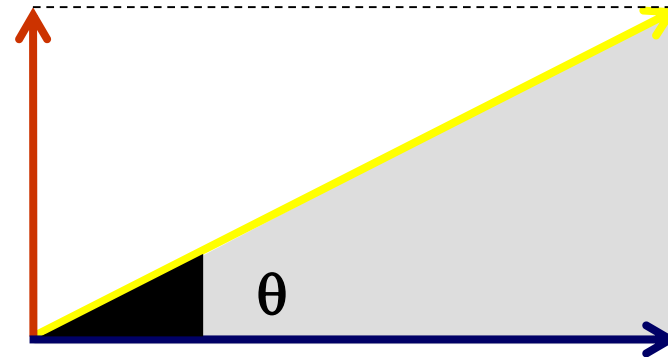



S, Total Power
(kVA)

P, Active Power
(kW)

Why Full Compensation is not Worthwhile ?

Full compensation is not worthwhile, since compensation beyond 0.95 p.f. requires unnecessarily large and expensive capacitive banks.

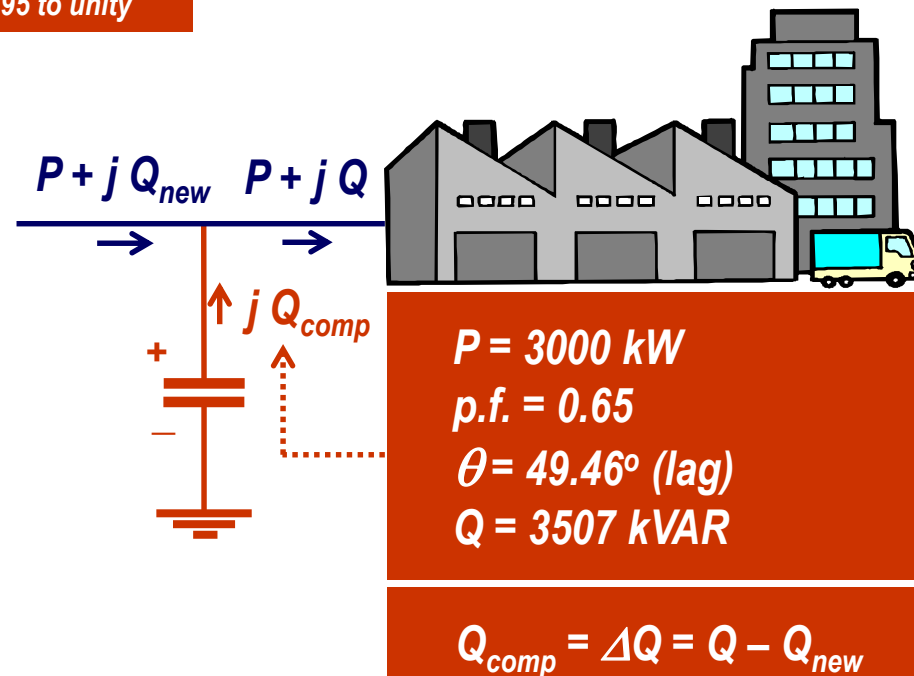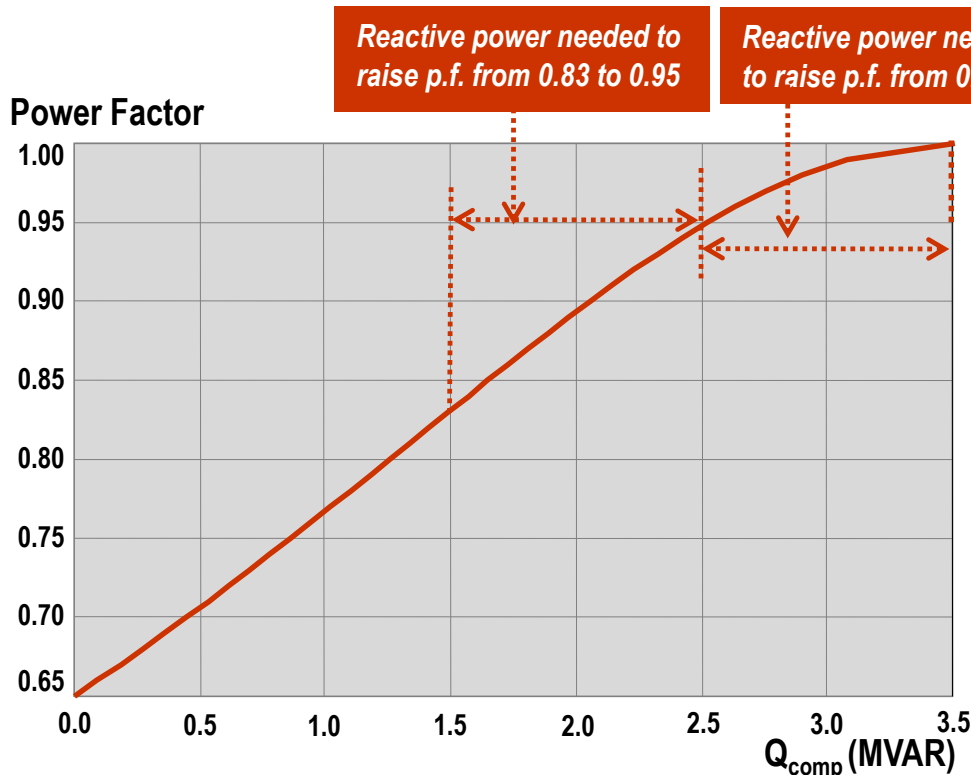Reactive power needed to raise p.f. from 0.95 to 1 is the same as that for raising p.f. from 0.83 to 0.95 (not worthwhile)



Application of Reactive Power Compensation

Reduction of Equipment Loading

- Transformers
- Lines
- Cables

are priced with respect to the power rating (kVA)

Prices of these equipments on the other hand, are determined by the cross-section (mm^2) of the equipment

Cross Section (mm^2)	Current Capacity (Amp)
1.0	12.0
1.5	16.0
2.5	21.0
4.0	27.0
6.0	35.0
10.0	48.0
16.0	65.0
25.0	88.0
35.0	110.0
50.0	140.0
70.0	175.0
95.0	215.0
120.0	225.0



Cross section (size) of the cable (mm^2)



Application of Reactive Power Compensation

Reduction of Equipment Loading

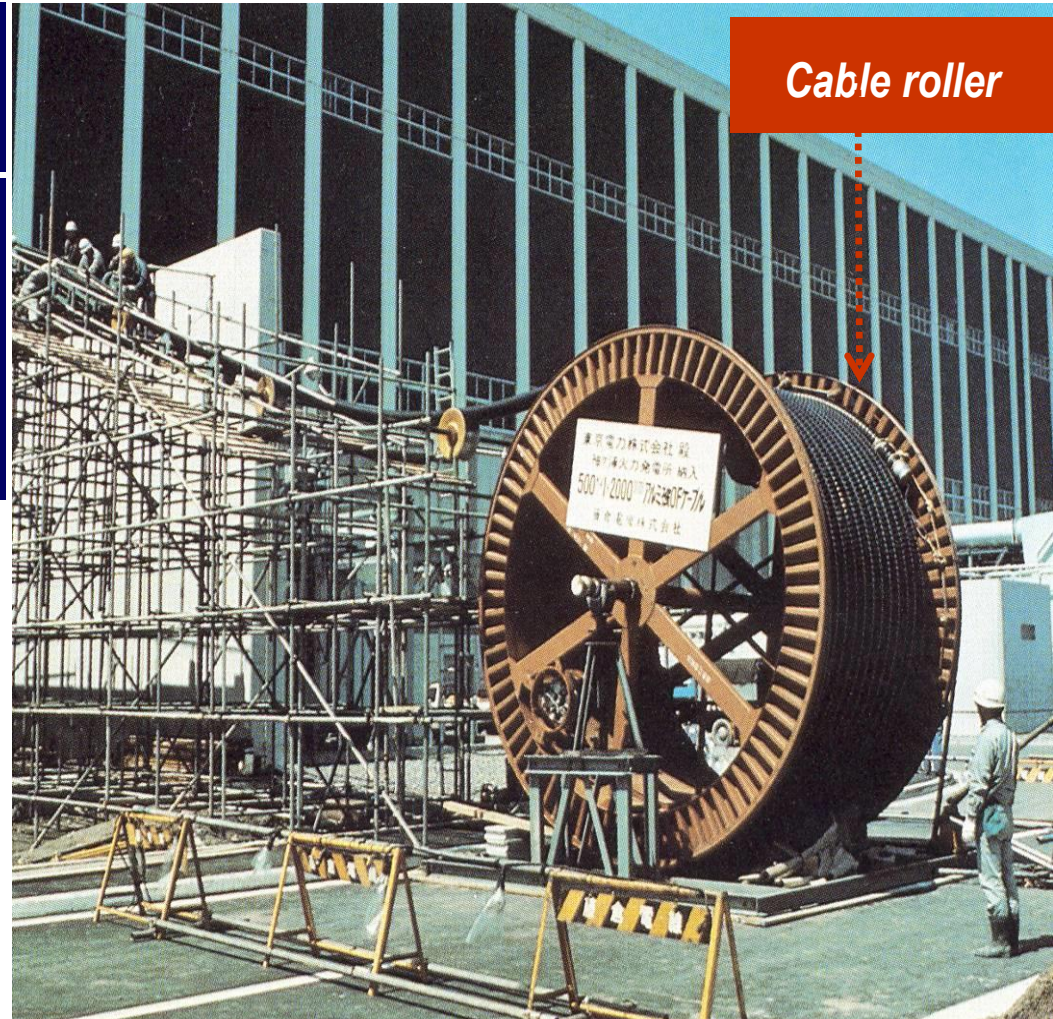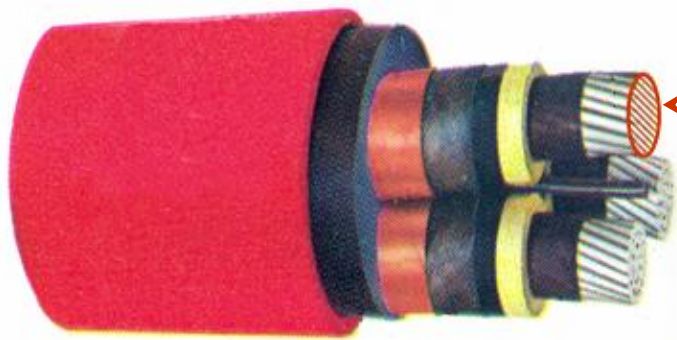Hence, the power rating S (kVA) of a cable is merely determined by the cross section, which must be minimized in order to reduce the investment to be made for the cable





Application of Reactive Power Compensation

Reduction of Equipment Loading

Hence, the power rating S (kVA) of a cable is merely determined by the cross section, which must be minimized in order to reduce the investment to be made for the cable

Hence, S (kVA) must be minimized

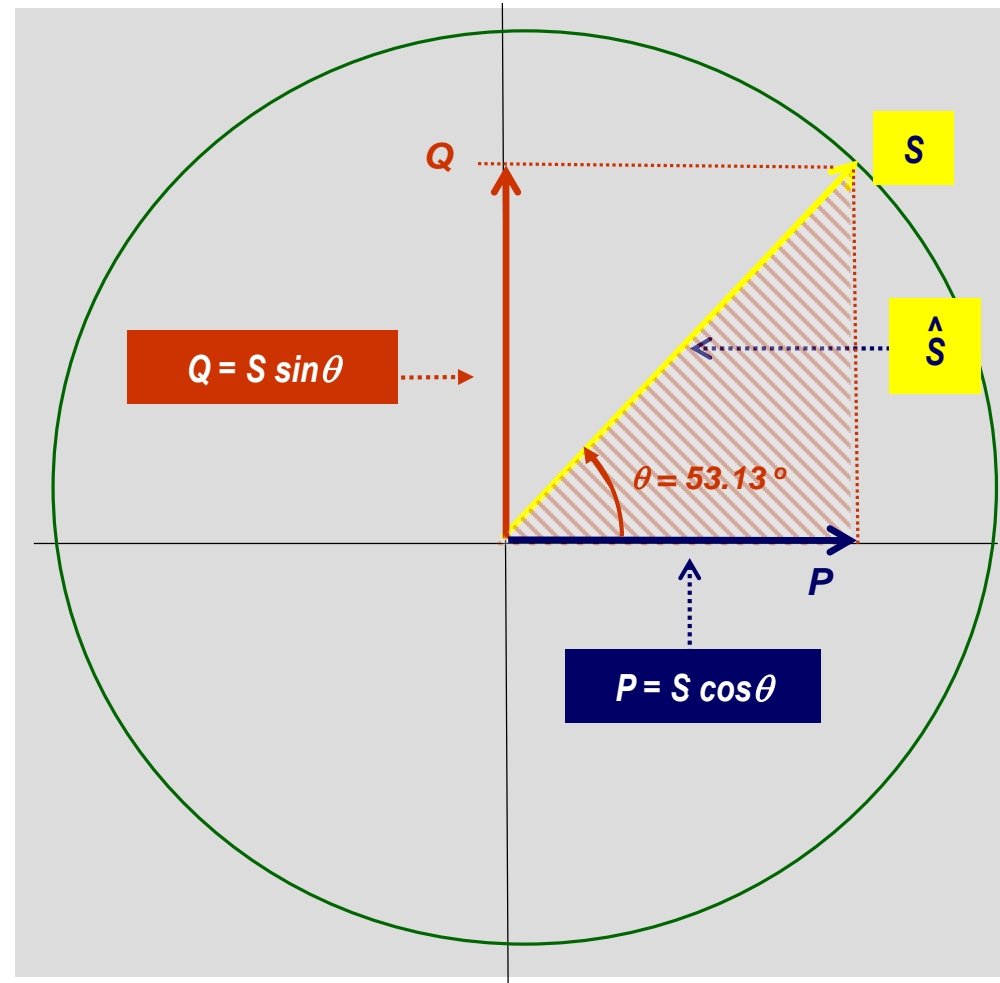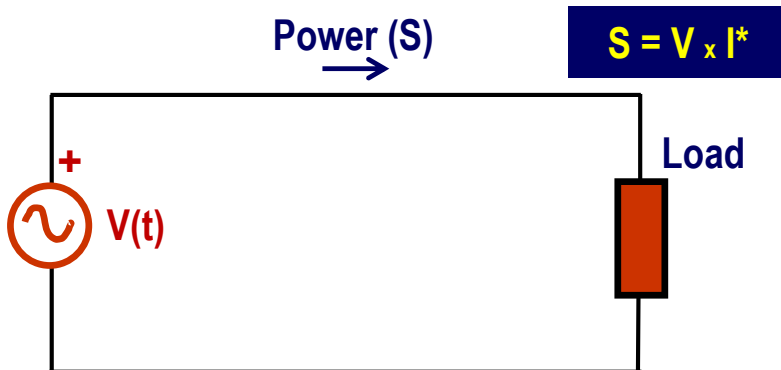

Alternative Ways of Reducing S (kVA)

Alternative Ways of Reducing S (kVA)

a) Reducing the overall loading;



$P + jQ$ (kW + j kVAR) (Overall consumption)

Unreasonable, unacceptable, since the active consumption (P) is determined only with respect to the needs of the consumer

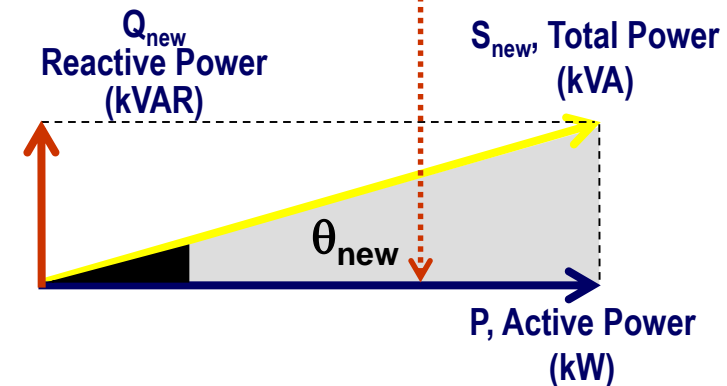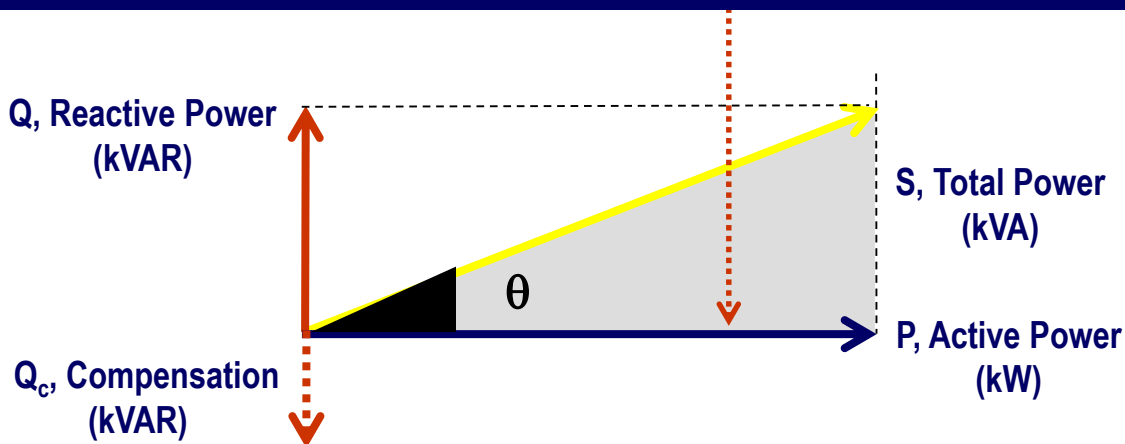a) Reducing only Q (kVAR) Possible, reasonable



Please note that active power remains unchanged after compensation



Example


Question

The factory shown on the RHS draws a load at 6300 V nominal voltage


$$P + jQ = 120 \text{ kW} + j 140 \text{ kVAR}$$

Calculate the amount of reactive power needed in order to raise the power factor of the factory to 0.95 (Lagging)

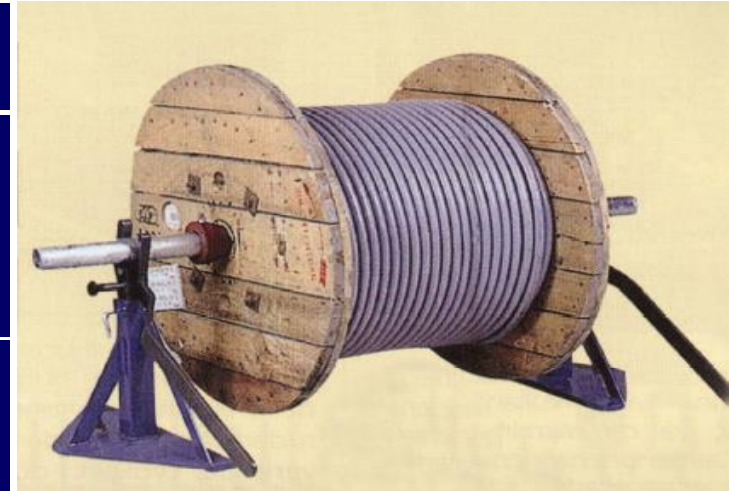(Although the system shown on the RHS is obviously three-phase, for simplicity in solution, it is assume here, to be single-phase)



TEDAŞ 6300 V (rms) Mains

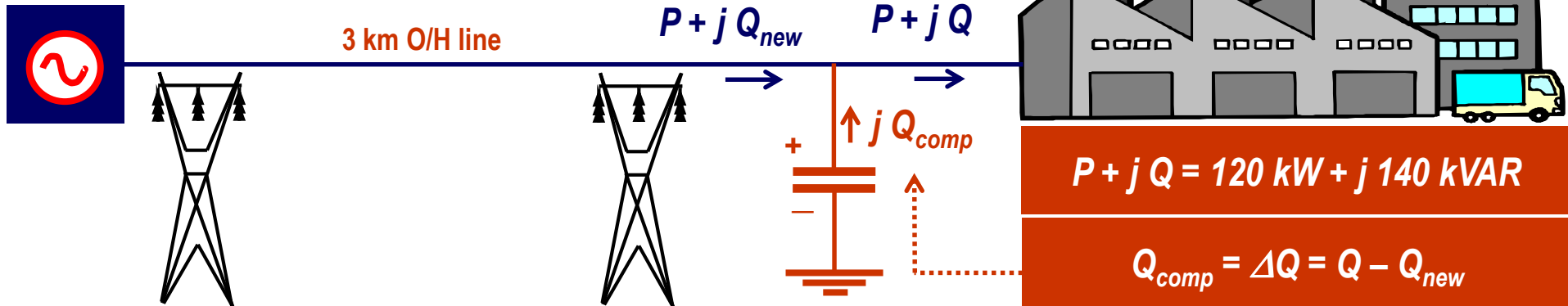

Example



Answer

Uncompensated (Given) Case

$$\begin{aligned}\tan \theta &= Q / P \\ &= 140 / 120 = 1.1667 \\ \theta &= \tan^{-1} 1.167 = 49.40^\circ \\ \text{p.f.: } \cos \theta &= 0.65 \text{ (lagging)}\end{aligned}$$

Compensated Case
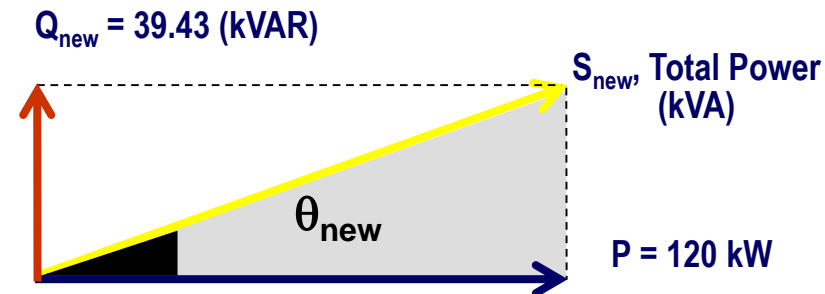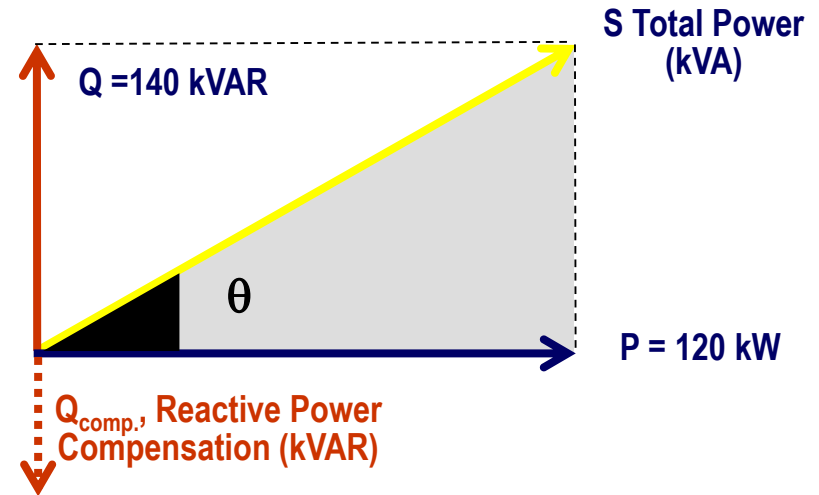
$$\begin{aligned}\cos \theta_{\text{new}} &= 0.95, \\ \theta_{\text{new}} &= \cos^{-1} 0.95 = 18.19^\circ \\ \tan \theta_{\text{new}} &= \tan 18.19^\circ = 0.3286 \\ \tan \theta_{\text{new}} &= Q_{\text{new}} / P \rightarrow Q_{\text{new}} = 0.3286 \times P \\ &= 39.43 \text{ kVAR} \\ Q_{\text{comp}} &= \Delta Q = Q - Q_{\text{new}} = 140 - 39.43 = 100.57 \text{ kVAR}\end{aligned}$$




Example

Question

Now, for the previous problem, calculate the reduction in line losses as a result of this compensation by assuming that line impedance is

$$R + jX = 10 + j20 \text{ Ohms}$$

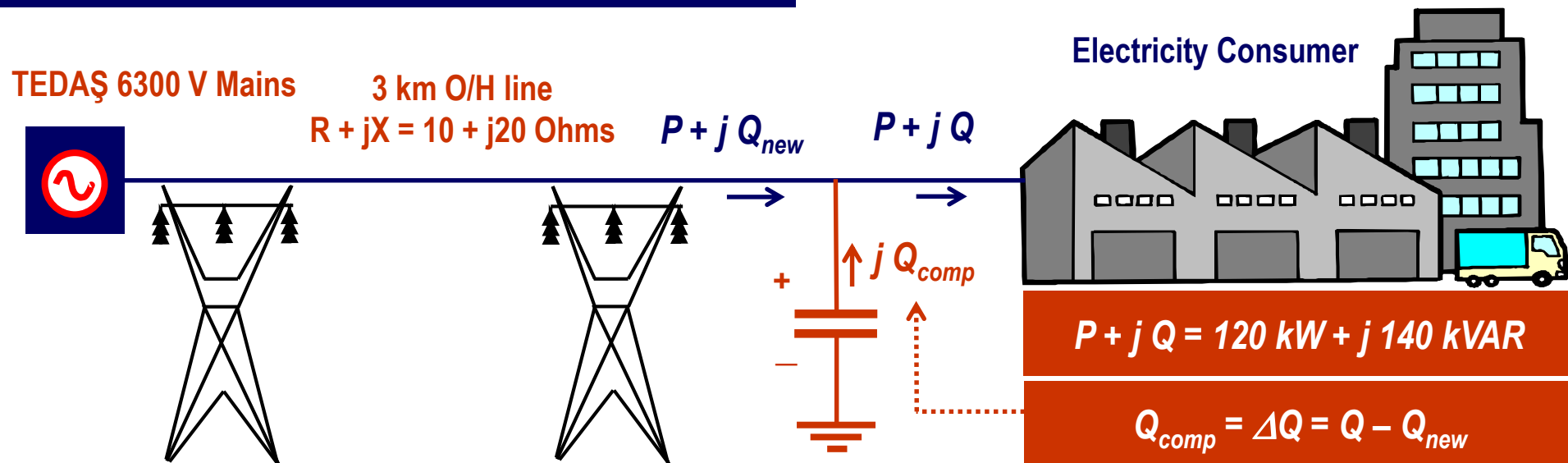

Example

$$S = VI^* \rightarrow I = S / V = \sqrt{120^2 + 140^2} / 6300 \\ = 184.39 \times 1000 / 6300 = 29.268 \text{ Amp}$$


$$S_{\text{new}} = VI_{\text{new}}^* \rightarrow I_{\text{new}} = \sqrt{120^2 + 39.43^2} / 6300 \\ = 126.312 \times 1000 / 6300 = 20.049 \text{ Amp}$$

$$P_{\text{loss}} = RI^2 = 10 \times 29.268^2 = 8566.39 \text{ Watts}$$


$$P_{\text{loss-new}} = RI_{\text{new}}^2 = 10 \times 20.049^2 = 4019.84 \text{ Watts}$$

$$\Delta P_{\text{loss}} = 8566.39 - 4019.84 \\ = 4546.55 \text{ Watts}$$

TEDAŞ 6300 V Mains

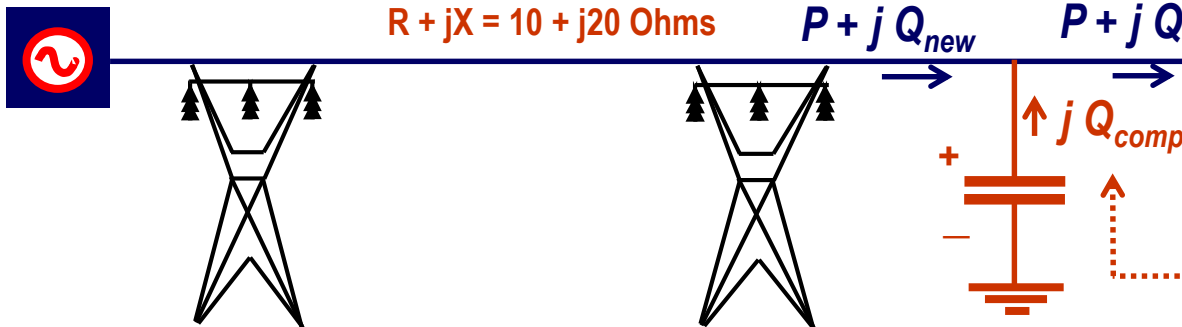

Electricity Consumer

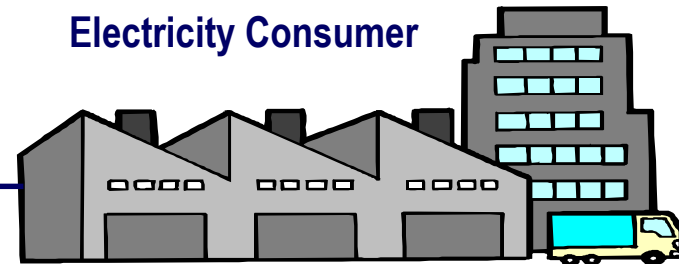


$$P + jQ = 120 \text{ kW} + j140 \text{ kVAR}$$

$$Q_{\text{comp}} = \Delta Q = Q - Q_{\text{new}}$$

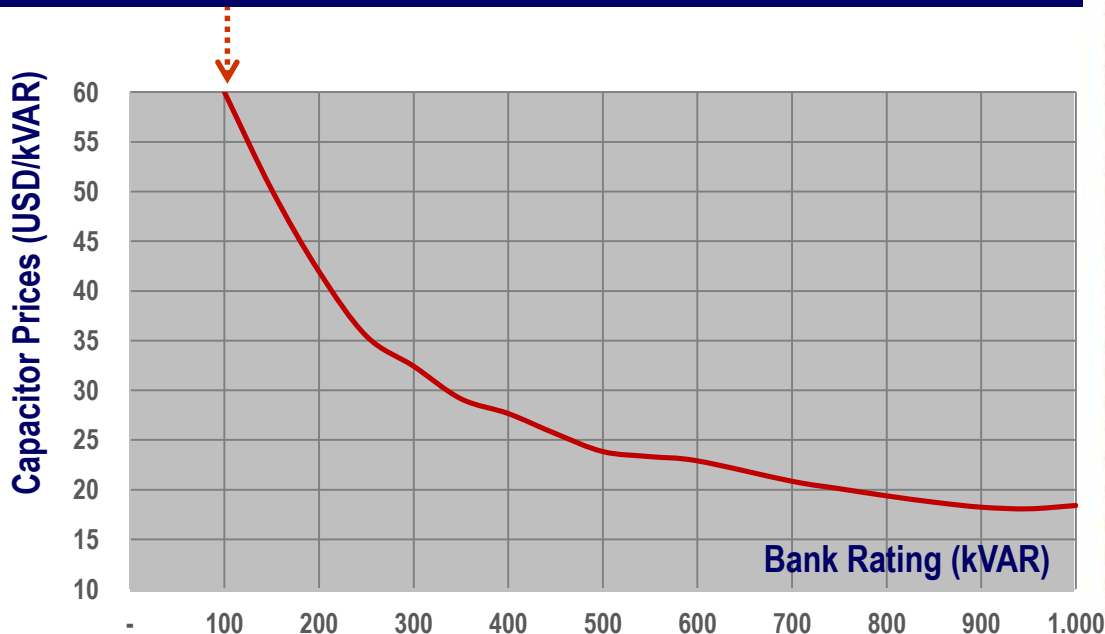Example

Now, calculate the return rate of the investment to be made for the compensator, by assuming that the retail price of electricity is 16 US Cents/kWh and the price of capacitor is **60 USD / kVAR** for a 100 kVAR bank



Capacitor Prices (USD/kVAR)

LV-ACB		List Price	
Low Voltage Automatic Capacitor Banks			
480 VOLT AUTOMATIC CAPACITOR BANKS			
BANK RATING (KVAR)	STEP X KVAR	MODEL NUMBER	LIST PRICE
150	3 X 50	150LVA480F2B	\$7,526
200	4 X 50	200LVA480F2B	\$8,389
250	5 X 50	250LVA480F2B	\$8,864
300	6 X 50	300LVA480F2B	\$9,727
350	7 X 50	350LVA480F2B	\$10,202
400	4 X 100	400LVA480F2B100	\$10,580
400	8 X 50	400LVA480F2B	\$11,065
450	9 X 50	450LVA480F2B	\$11,540
500	5 X 100	500LVA480F2B100	\$11,918
500	10 X 50	500LVA480F2B	\$12,404
550	11 X 50	550LVA480F2B	\$12,830
600	6 X 100	600LVA480LV2B100	\$13,256
600	12 X 50	600LVA480LV2B	\$13,742
650	13 X 50	650LVA480LV2B	\$12,280
700	7 X 100	700LVA480F2B100	\$14,594
700	14 X 50	700LVA480F2B	\$15,080
750	15 X 50	750LVA480LV2B	\$15,506
800	8 X 100	800LVA480LV2B100	\$15,933
800	16 X 50	800LVA480F2B	\$16,418
900	9 X 100	900LVA480F2B100	\$17,174
1000	10 X 100	1000LVA480F2B100	\$18,414

Example

Calculation of the Return Rate

$$\begin{aligned}\Delta P_{\text{loss}} &= 8566.39 - 4019.84 = 4,546.55 \text{ Watts} \\ \text{Investment} &= 100.57 \text{ kVAR} \times 60.00 \text{ USD/kVAR} \\ &= 6.034,20 \text{ USD} \\ \text{Saving / hour} &= 4,546.55 / 1000 \text{ kW} \times (16 / 100 \text{ USD}) \\ &= 0,7274 \text{ USD / hour} \\ \text{Return Rate} &= \text{Investment} / (\text{Saving / hour}) \\ &= 6.034,20 / 0.7274 \\ &= 8,295.57 \text{ hours} = 345.45 \text{ days} \\ &= 0.95 \text{ years}\end{aligned}$$

Three - Phase Compensator Bank



Example

Question


Now, for the previous problem, determine the cross sections of the line for the alternative cases, when line is compensated and uncompensated

$$I_{new} = 20.495 \text{ Amp}$$

$$I_{initial} = 29.268 \text{ Amp}$$



TEDAŞ 6300 V
Mains

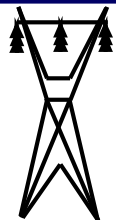3 km O/H line
 $R + jX = 1 + j2 \text{ Ohms}$



$P + jQ_{new}$

$P + jQ$

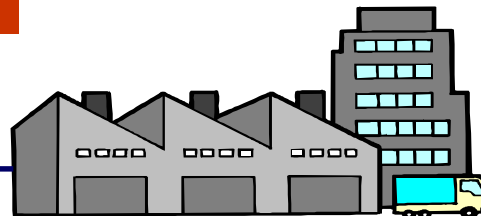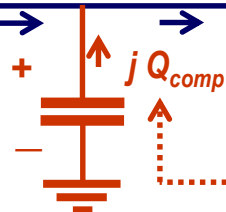

$$P + jQ = 120 \text{ kW} + j140 \text{ kVAR}$$

$$Q_{comp} = \Delta Q = Q - Q_{new}$$

Cheaper alternative



Electricity Consumer

Cross Section (mm ²)	Current Capacity (Amp)
1.0	12.0
1.5	16.0
2.5	21.0
4.0	27.0
6.0	35.0
10.0	48.0
16.0	65.0
25.0	88.0
35.0	110.0
50.0	140.0
70.0	175.0
95.0	215.0
120.0	225.0

Question

Question

Now, for the previous problem, calculate the shunt capacitance in Farads needed for the amount of compensation found above

$$Q_{comp} = \Delta Q = Q - Q_{new} = 140 - 39.43 = 100.57 \text{ kVAR}$$

$$Q_{comp} = V I_{comp}^* \rightarrow I_{comp} = Q_{comp} / V = 100570 \text{ VA} / 6300 \text{ V} = 15.963 \text{ Amp}$$

$$X_{comp} = V / I_{comp} = 6300 / 15.963 = 394.65 \text{ Ohms}$$


$$X_{comp} = 1 / (j\omega C)$$

$$C = 1 / (j\omega X) = 1 / (314.15 \times 394.65) = 123.98 \text{ mF}$$

$$Q_{new} = Q + Q_{comp}$$

$$Q_{comp} < 0$$

Electricity Consumer

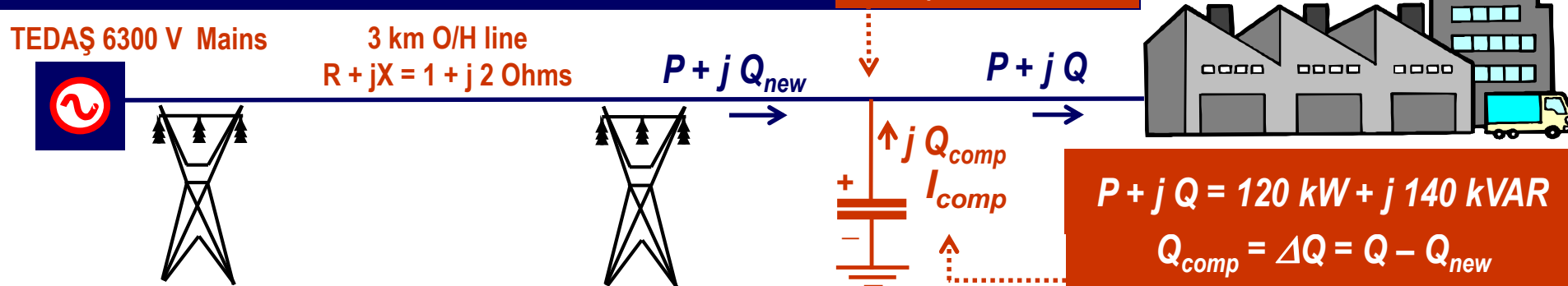

Medium Voltage Capacitor Banks

Shunt connection of large capacity capacitors in power systems



Installation of MV Capacitor Banks



LV (Low Voltage) Capacitor Banks




Contactors

Fuses

Capacitor Bank



Electronic Capacitors in a Motherboard

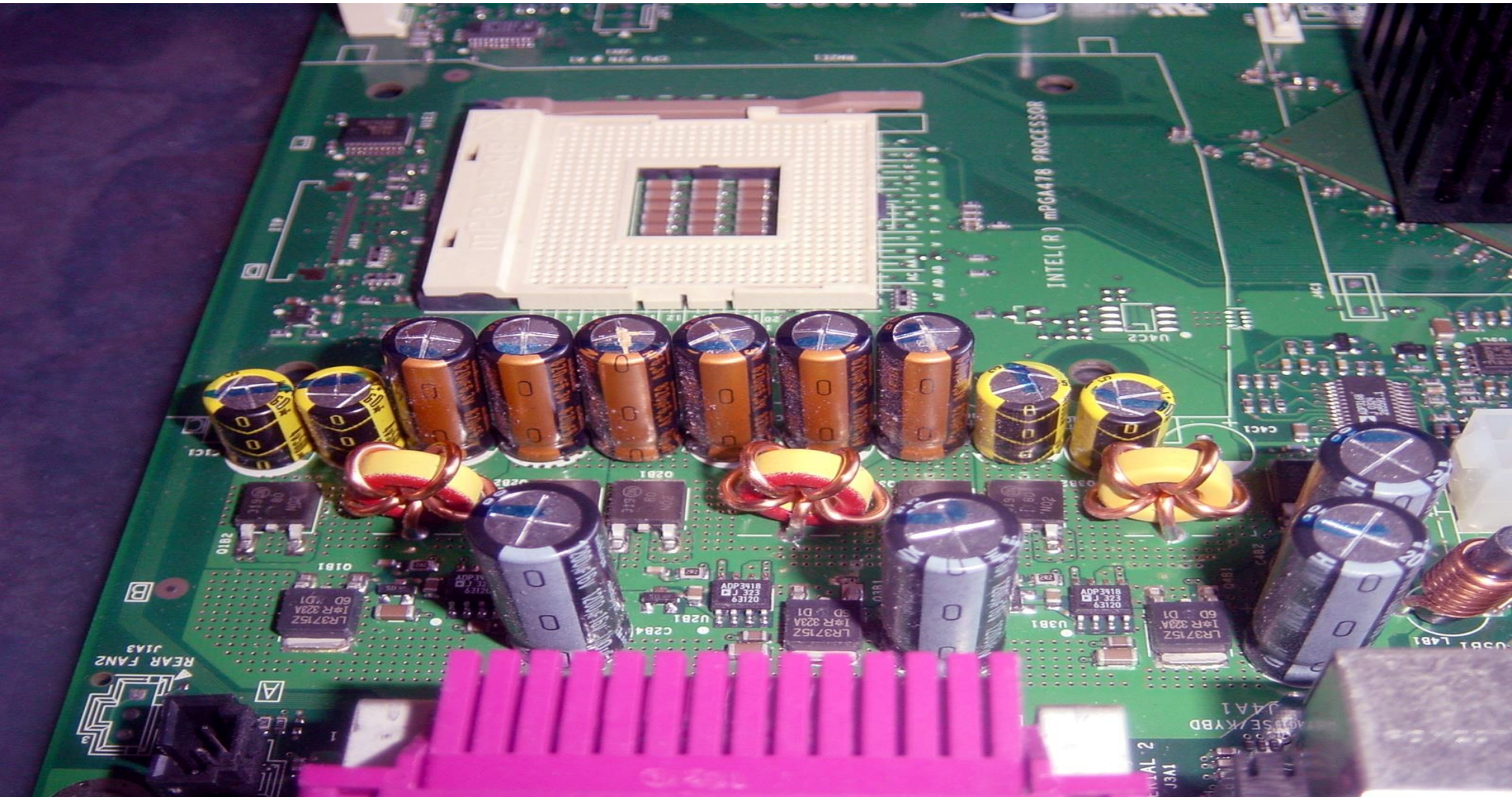

Another Example

- Early in the history of electricity, Thomas Edison's General Electric company was distributing DC electricity at 110 volts in the United States.
- Then Nikola Tesla devised a system of three-phase AC electricity at 240 volts. Three-phase meant that three alternating currents slightly out of phase were combined in order to even out the great variations in voltage occurring in AC electricity. He had calculated that 60 cycles per second or 60Hz was the most effective frequency. Tesla later compromised to reduce the voltage to 110 volts for safety reasons.

Another Example

Europe goes to 50 Hz:

With the backing of the Westinghouse Company, Tesla's AC system became the standard in the United States. Meanwhile, the German company AEG started generating electricity and became a virtual monopoly in Europe. They decided to use 50 Hz instead of 60 Hz to better fit their metric standards, but they kept the voltage at 110 V.

Another Example

Unfortunately,

- 50 Hz AC has greater losses and is not as efficient as 60 HZ.
- Due to the slower speed, 50Hz electrical generators are 20 % less effective than 60Hz generators. Electrical transmission at 50 Hz is about 10-15 % less efficient. 50Hz transformers require larger windings and 50 Hz electric

Another Example

Europe goes to 220 V

Europe stayed at 110 V AC until the 1950s, just after World War II. They then switched over to 220 V for better efficiency in electrical transmission. Great Britain not only switched to 220 V, but they also changed from 60Hz to 50 Hz to follow the European lead. Since many people did not yet have electrical appliances in Europe after the war, the change-over was not that expensive for them.

Another Example

U.S. stays at 110 V, 60Hz

The United States also considered converting to 220 V for home use but felt it would be too costly, due to all the 110 V electrical appliances people had. A compromise was made in the U.S. in that 220 V would come into the house where it would be split to 110 V to power most appliances. Certain household appliances such as the electric stove and electric clothes dryer would be powered at 220 V.

Did everybody follow this part carefully ?

